

Code: 13A02101

B.Tech II Year I Semester (R13) Regular &amp; Supplementary Examinations December 2015

**ELECTRICAL CIRCUITS**  
(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- The current in a 15 mH inductor is  $i_L = (2 - e^{-1000t})$  mA. What is the voltage across inductor?
  - Define reluctance and magnetic flux.
  - Define power factor. What is its significance?
  - Write any four advantages of three phase (3- $\Phi$ ) system.
  - What are the properties of resonance of RLC series circuit?
  - What is meant by oriented graph?
  - State reciprocity theorem.
  - Define two port network.
  - State initial and final value theorems.
  - Define even symmetry and odd symmetry.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 (a) If  $R_1$ ,  $R_2$  and  $R_3$  are connected in star and  $R_{12}$ ,  $R_{23}$  and  $R_{31}$  are connected in delta, obtain the expressions for star-delta and delta-star equivalence of resistive network.
- (b) Two 100 W, 220 V bulbs are required to be connected across a 400 V supply. Find the value of the resistance to be inserted in the line so that the voltage across the bulbs does not exceed 220 V.

**OR**

- 3 (a) Derive the relation between self inductance, mutual inductance and coefficient of coupling.
- (b) Two coupled coils have  $K = 0.8$ ,  $N_1 = 500$  turns,  $N_2 = 1000$  turns and the mutual flux being 0.9 Wb, find the primary coil flux. If the primary current be 10 A, find the primary coil inductance. Also obtain the secondary inductance.

**UNIT – II**

- 4 (a) Define and derive the expressions for a sinusoidal wave excited by an AC source: (i) Average value. (ii) RMS value. (iii) Form factor.
- (b) 100 V, 50 Hz is applied across a series RLC circuit having  $R = 10 \Omega$ ,  $L = 100$  mH and  $C = 1000 \mu\text{F}$ . Find the current and drop across each element.

**OR**

- 5 (a) Derive the relationship between phase and line values in a three phase balanced star connected system.
- (b) The power readings of two watt meters are +15 kW and -4 kW for a three phase load. If the supply voltage is balanced 440 V, find the true power drawn by the load, the power factor and line current.


Contd. in page 2

## UNIT – III

- 6 (a) Derive the relation between bandwidth, resonant frequency and Q-factor of a series circuit.  
 (b) The Q-factor of a RLC circuit is 5 at its resonance frequency of 1 kHz. Assuming the power dissipation of 250 W, when the current drawn is 1 A, find the circuit parameters. Determine the BW of the circuit.


OR

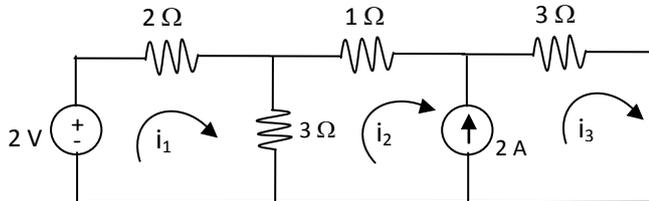- 7 (a) Explain the principle of duality and construction of a dual network.  
 (b) Calculate the mesh currents in the network shown in figure below.


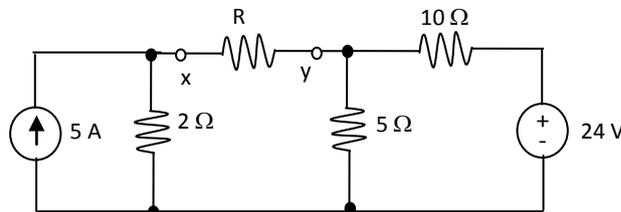
## UNIT – IV

- 8 (a) Show that the efficiency is 50% during maximum power transfer condition.  
 (b) What would be the value of R such that maximum power transfer can take place from the rest of the network to R in figure given below? Obtain the amount of this power.



OR

- 9 (a) Prove that the overall ABCD parameters in matrix for cascade connected of two-port is the matrix products of ABCD parameters for each individual two-port network.  
 (b) Following short circuit currents and voltages are obtained experimentally for a two-port network:  
 (i) With output short-circuited,  $I_1 = 5 \text{ mA}$  ;  $I_2 = -0.3 \text{ mA}$  ;  $V_1 = 25 \text{ V}$ .  
 (ii) With input short-circuited ,  $I_1 = -5 \text{ mA}$  ;  $I_2 = 10 \text{ mA}$  ;  $V_2 = 30 \text{ V}$ .  
 Determine Y – parameters.

## UNIT – V

- 10 (a) Explain the properties of Fourier transform.  
 (b) Explain line spectra and phase angle spectra of Fourier series.

OR

- 11 (a) Derive the expression for current of RL series circuit excited with the DC supply.  
 (b) In a series R-L-C circuit,  $R = 5 \Omega$ ,  $L = 1 \text{ H}$  and  $C = 1 \text{ F}$ . A d.c voltage of 20 V is applied at  $t = 0$ . Obtain  $i(t)$ .

\*\*\*\*\*