

B.Tech IV Year I Semester (R13) Supplementary Examinations June 2017

**SWITCHED MODE POWER CONVERTERS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*


- 1 Answer the following: (10 X 02 = 20 Marks)
- Explain the principle of volt second balance in inductors.
  - Obtain the input-output voltage as a function of duty ratio for a Buck-Boost dc-dc converter in continuous conduction mode.
  - List out the difference between fly back and push pull topologies.
  - Discuss why transformer isolations are needed in high frequency power conversion.
  - List the various classifications of resonant converters.
  - What is meant by zero voltage switching?
  - Explain the significance of small signal modeling in DC-DC converters.
  - List out the dynamic performance indices of DC-DC converters.
  - List out the controller specifications.
  - Why, frequency domain analysis is important in controller design?

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

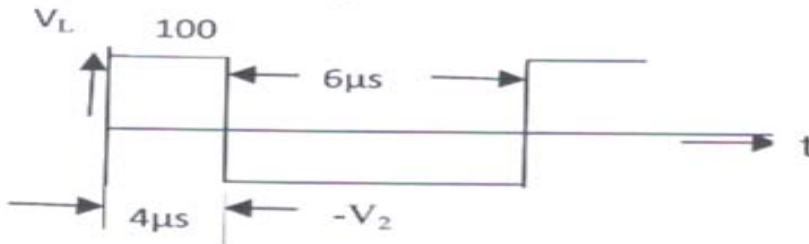**UNIT – I**

- 2 (a) Illustrate the operation of step down converter in continuous conduction mode and derive an expression for the ripple voltage.  
(b) Calculate  $V_2$  for a given wave form in DC steady state.



OR

- 3 Explain the operation of CUK converter and derive output voltage equation.

**UNIT – II**

- 4 (a) Draw the circuit and explain the operation of fly back converter.  
(b) Compare Isolated and non-isolated switched mode converters.

OR

- 5 Draw the circuit diagram and explain the operation of a full bridge push pull converter and draw the load current and load voltage waveform.

**UNIT – III**

- 6 Discuss the operation of parallel resonant dc-dc converter with the help of circuit diagram.

OR

- 7 Analyze and obtain the output voltage of L - type boost converter.

**UNIT – IV**

- 8 Obtain the steady state solution of the non-ideal boost converter by using its average model.

OR

- 9 Obtain the transfer function of buck converter using its equivalent circuit.

**UNIT – V**

- 10 Discuss about the controller specifications for design of controller.

OR

- 11 Explain about the design of proportional, Integral and derivative controller.

\*\*\*\*\*