

NETWORK ANALYSIS

(Electronics and Communication Engineering)


Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) Give the properties of Miller and Tellegen’s theorem.
 - (b) Explain the concept of parallel convention 2, two-port networks.
 - (c) The s-domain function $G(S) = \frac{S+1}{S(S+2)}$. Find the initial value of g(t).
 - (d) The number of turns of a coil having a time constant “t” are doubled. What will be the new time constant?
 - (e) In the series circuit shown below for the series resonance at the value of the coupling coefficient “k” will be.

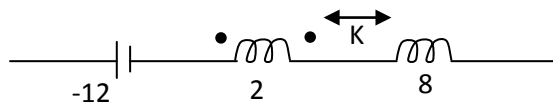


- (f) The impedance function of a parallel RLC circuit has poles located at $-3 \pm j4$ rad/sec. If the value of $L = 1H$, determine R.
- (g) Obtain the state model for the system describe by: $\ddot{Y} + 7\dot{Y} + 5Y = \ddot{u} + 3\dot{u} + 2u$.
- (h) Explain the advantage of state variable analysis.
- (i) Define characteristic impedance “ Z_0 ”.
- (j) Mention any two properties of symmetrical networks.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)


UNIT – I

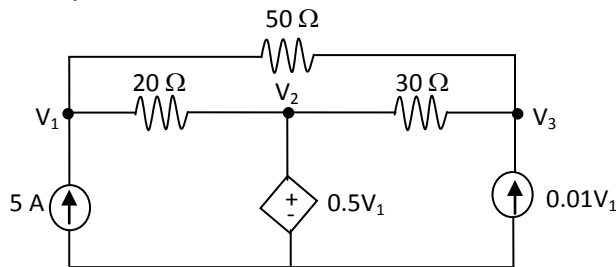- 2 (a) Explain the properties of cut-set, tie-set and incident matrix.
 (b) By using nodal analysis determine the V_1 and V_3 for the network shown below.



OR

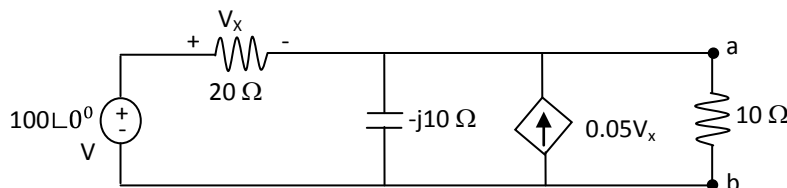- 3 (a) Find the current through 10 ohm resistor using Thevenin’s theorem for the given network.




- (b) State and explain maximum power transfer theorem with a circuit excited by AC source.

Contd. in page 2

UNIT – II

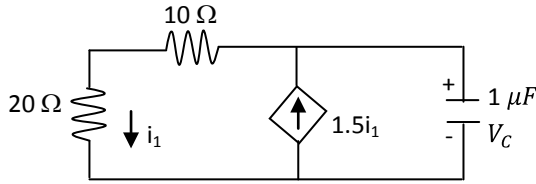
- 4 (a) Find the voltage labeled V_C for $t \geq 0$ if $V_C(0)$ is 2 V.



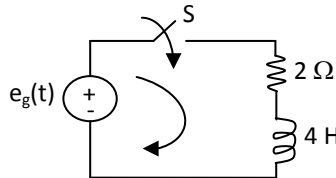- (b) Obtain the transient response of a RC circuit excited by sinusoidal input.

OR

- 5 (a) The circuit shown below, the voltage across the circuit is $e_g(t) = 2.5t$ volts. What are the values of $V_L(t)$ at 4 sec.




- (b) Explain the complex frequency plane and properties.

UNIT – III

- 6 (a) A RLC circuit comprising a 10 ohm resistance is to have a bandwidth of 100 rad/sec. determine the value of the capacitance to make the system to resonate at 400 rad/sec, selectivity if the resistance is altered to 50 ohms and what are the half power frequencies.
 (b) Explain the concept of modeling of coupled circuits.


OR

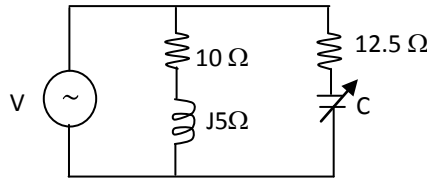- 7 (a) Derive the expression for energy stored in magnetic field.
 (b) Determine the value of capacitance C in order to resonant at 6366 Hz for the given circuit.



UNIT – IV

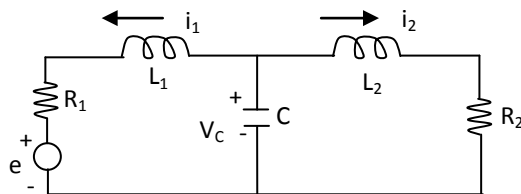
- 8 (a) Obtain the state space representation of RLC network.



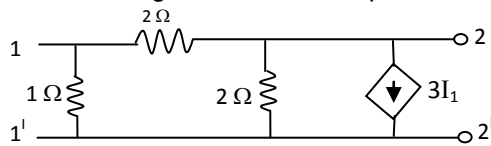- (b) Explain image parameters in two port network.

OR

- 9 (a) For the network shown in figure below, find z-parameters.



- (b) Obtain a state model of the systems described by the transferfunction $\frac{Y(s)}{U(s)} = \frac{5}{s^3 + 6s + 7}$.

UNIT – V

- 10 (a) Explain the analysis of prototype band stop filter. Derive the expression for pitch factor.
 (b) Design a constant K-pass filter having $f_c = 4$ kHz and design impedance $R_0 = 600$ ohms by using section.

OR

- 11 (a) Discuss about composite filters.
 (b) Design a T-section constant K-pass filter having a cut-off frequency of 10 Hz and design impedance $R_0 = 600$ ohms. Find the characteristic impedance and phase constant at 25 kHz.