

NETWORK ANALYSIS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)


- 1 Answer the following: (10 X 02 = 20 Marks)
- State the superposition.
 - Define incidence matrix.
 - Write the expression for transient current of RL circuit for a step input and draw the transient curve.
 - What do you mean by external critical frequency?
 - A two port network has the following Z parameters $Z_{11} = 10 \Omega$, $Z_{22} = 12 \Omega$, $Z_{12} = Z_{21} = 5 \Omega$. Find Y_{11} .
 - Define quality factor.
 - List the advantages of m- derived filters.
 - Draw the Frequency Vs Attenuation constant curve for a Prototype Band Pass Filter.
 - Test whether: $F(s) = \frac{5(s+1)^2}{s^3 + 2s^2 + 2s + 40}$ is positive real.
 - Write the equations that describe a two port network in terms of the transmission parameters.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 Find the value of RL in the circuit of shown below, such that the maximum power transfer takes place. Also calculate maximum power transferred.

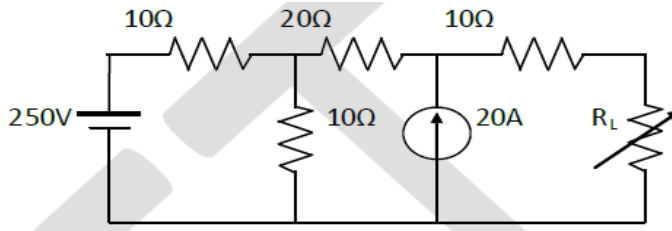**OR**

- 3 The reduced incidence matrix of an oriented graph is:

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

- (i) Draw the graph. (ii) Determine the Tie-set matrix.

UNIT – II

- 4 A series RLC circuit with $R = 300 \text{ ohms}$, $L = 1\text{H}$ and $C = 100 \text{ micro farads}$ has a constant voltage of 50 V applied to it at $t = 0$. Find the maximum current value. Assume zero initial conditions.

OR


- 5 Draw the pole zero diagram for the given network function and hence obtain $v(t)$.

$$V(s) = \frac{4(s+2)s}{(s+1)(s+3)}$$

Contd. in page 2

UNIT – III

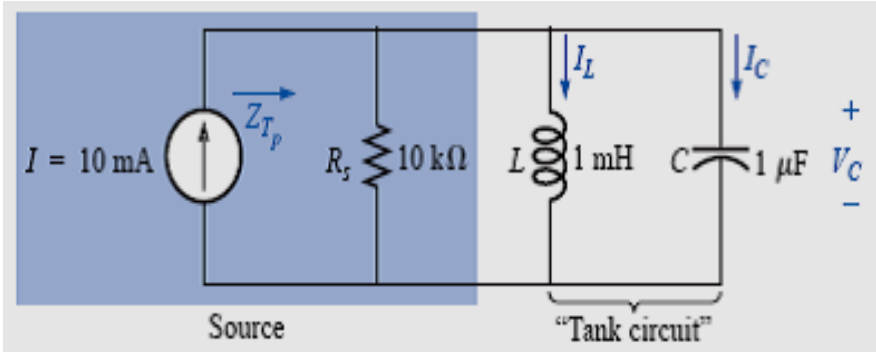- 6 (i) Determine the resonant frequency f_p .
 (ii) Find the total impedance at resonance.
 (iii) Calculate the quality factor, bandwidth, and cutoff frequencies f_1 and f_2 of the system.




OR

- 7 The bandwidth of a series resonant circuit is 400 Hz.
 (i) If the resonant frequency is 4000 Hz, what is the value of Q_s ?
 (ii) If $R = 10 \Omega$, what is the value of X_L at resonance?
 (iii) Find the inductance L and capacitance C of the circuit.


UNIT – IV

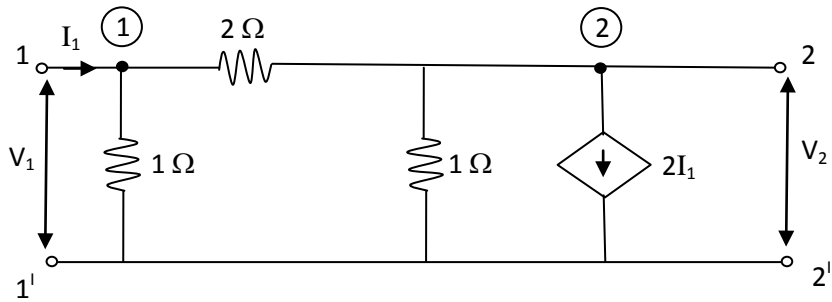- 8 Find the Z and Y parameters of the circuit shown below:



OR

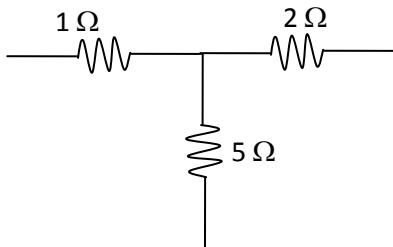- 9 Determine the image parameters of the network shown below.



UNIT – V

- 10 Design a prototype T section High Pass Filter with cut off frequency 10 KHz and nominal impedance 600 Ω.

OR

- 11 Design a m-derived π section Low Pass Filter having cut-off frequency of 1 KHz, design impedance of 400 Ω and the resonant frequency of 1100 Hz.
