

**NETWORK ANALYSIS**

(Electronics and Communication Engineering)

Time: 3 hours


Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*

1 Answer the following: (10 X 02 = 20 Marks)

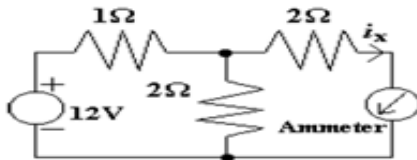(a) The value of  $i_x$  shown in following figure is:-----




- (b) Define Tree and Co-Tree.
- (c) Write the limitations of superposition theorem.
- (d) A network N is to be connected to load of 500 ohms. If the Thevenin's equivalent voltage and Norton's equivalent current of N are 5 volts and 10mA respectively, calculate the current through the load.
- (e) The Q-factor of a parallel resonance circuit consisting of an inductance of value 1mH, capacitance of value  $10^{-5}$  F and a resistance of 100 ohms is.
- (f) Define resonant frequency.
- (g) Define Reciprocity theorem.
- (h) Explain maximum power transfer theorem.
- (i) What do you mean by the state? What are state variables?
- (j) Write the applications of different types of filters?

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

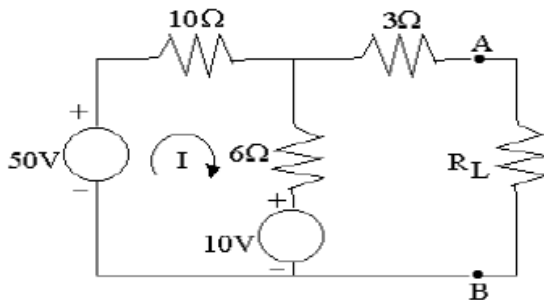
**UNIT – I**

2 Obtain the Thevenin's equivalent of the network shown in figure below. Then draw the Norton's equivalent network by source transformation.



OR

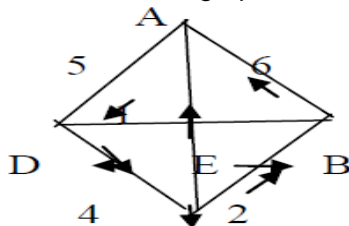3 (a) For the directed graph shown below obtain the cut set matrix.




(b) State and prove superposition theorem and Millman's theorem.

Contd. in page 2
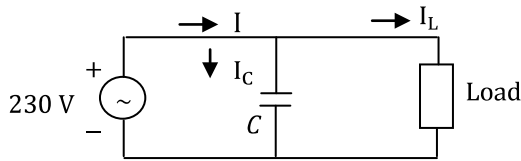
## UNIT – II

- 4 (a) An inductive coil, having resistance of  $8 \Omega$  and inductance of  $80 \text{ mH}$ , is connected in series with a capacitance of  $100 \mu\text{F}$  across  $150 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate: (i) The current. (ii) The power factor. (iii) The voltages drop in the coil and capacitance respectively.
- (b) The power consumed in the inductive load as shown in figure below is  $2.5 \text{ kW}$  at  $0.71$  lagging power factor (pf). The input voltage is  $230 \text{ V}$ ,  $50 \text{ Hz}$ . Find the value of the capacitor  $C$ , such that the resultant power factor of the input current is  $0.866$  lagging.



OR

- 5 (a) Derive RMS value of alternating quantity from fundamentals
- (b) A  $50 \text{ Hz}$  sinusoidal voltage applied to a single phase circuit has its RMS value of  $200 \text{ V}$ , its value at  $t = 0$  is  $28.3$  volts positive. The current drawn by the circuit is  $5 \text{ A}$  r.m.s and lags behind the voltage by one sixth of a cycle. Write the expressions for instantaneous values of voltage and current.

## UNIT – III


- 6 (a) Derive the expressions of quality factor using the general definition and show that greater the quality smaller the band width, using current Vs angular frequency plot for various values.
- (b) Consider a series resonance circuit consisting of a  $10 \text{ ohms}$  resistance, a  $2 \text{ mH}$  inductance and a  $200 \text{ nF}$  capacitance. Determine the maximum energy stored, the energy dissipated per cycle of the circuit.

OR


- 7 (a) Define coefficient of magnetic coupling. Derive the expression for coefficient of magnetic coupling.
- (b) Write the properties of ideal transformer and analyze ideal transformer.
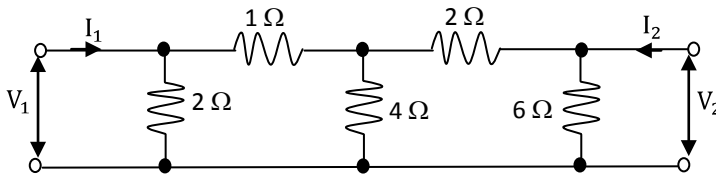
## UNIT – IV

- 8 (a) Find the y-parameters for the network shown in figure below.




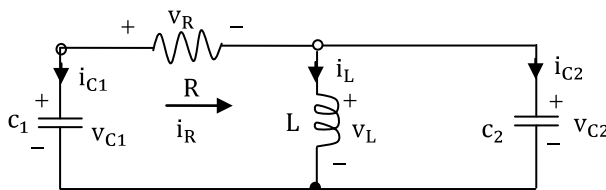- (b) Form the state matrix equation for the network shown in figure below.



OR

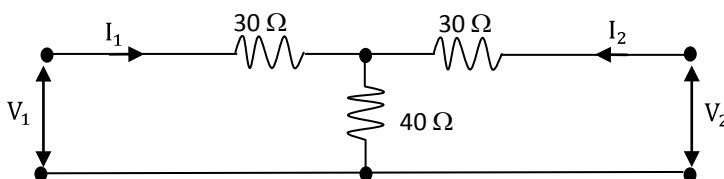- 9 For the symmetrical 2-port network shown in figure below, find the z-and ABCD-parameters.



## UNIT – V

- 10 (a) State and explain the characteristics of passive filter
- (b) Design a T-section constant K-high pass filter having cut-off frequency of  $10 \text{ kHz}$  and design impedance  $R_0 = 600 \Omega$ . Find its characteristic impedance and phase constant at  $25 \text{ kHz}$ .

OR

- 11 (a) Explain briefly about M-derived high pass filter.
- (b) Design an M-derived high pass filter having a design impedance of  $600 \Omega$ , cut off frequency of  $5 \text{ kHz}$  and  $m = 0.35$ . Also determine the frequency of infinite attenuation.

\*\*\*\*\*