

DIGITAL LOGIC DESIGN

(Common to IT and CSE)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- If $1010_2 + 10_2 = X_{10}$, then X is ----
 - Write the first 9 decimal digits in base 3.
 - What is meant by don't care condition?
 - Why AND and OR are not universal gates? Give the reason.
 - Write the truth table of half subtractor.
 - Implement AND gate using only two input NOR gates.
 - Write the truth table of clocked T-Flip flop.
 - Where the ripple counter is used?
 - What is the function of EAROM?
 - Mention few applications of PAL.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT - I

- 2 (a) Obtain the truth table for the function $F = xy + xy' + y'z$
 (b) Prove that the sum of all minterms of a Boolean function for three variables is 1.
- OR
- 3 (a) Show that the dual of the exclusive-OR is equal to its complement
 (b) Convert the decimal number 1973 to base 3, base 5 and base 7.

UNIT - II

- 4 Simplify the following Boolean expressions using K-map and implement them using NAND gates:
 $F(W, X, Y, Z) = XZ + WXY + WXY + WYZ + WYZ$.
- OR
- 5 Simplify the following expression using tabulation method:
 $F(A, B, C, D, E) = \sum (4, 6, 7, 9, 11, 12, 13, 14, 15, 20, 22, 25, 27, 28, 30) + d(1, 5, 29, 31)$.

UNIT - III

- 6 (a) How full adder is different from full subtractor? Explain.
 (b) Draw and explain various implementations of full adder.
- OR
- 7 (a) What is the function of magnitude comparator? Explain with an example.
 (b) Design a combinational circuit with four input lines that represent a decimal digit in BCD and four output lines that generate the 9's complement of the input digit.

UNIT - IV

- 8 (a) Draw the block diagram of sequential circuit. Explain.
 (b) What is state assignment? Explain with a suitable example.
- OR
- 9 (a) Draw the basic flip flop circuit with NOR gates. Explain its operation.
 (b) Explain about 3-bit binary counter with a suitable logic diagram.

UNIT - V

- 10 (a) Compare PAL and PLA with respect to various performance features.
 (b) Explain about TTL family.

- OR
- 11 (a) Explain about memory decoding error detection and correction.
 (b) What is the importance of ECL family? Explain.
