

B.Tech II Year II Semester (R13) Supplementary Examinations May/June 2017

**PULSE & DIGITAL CIRCUITS**

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- Sketch the waveforms of input and output when symmetrical square wave is applied to ideal integrator.
  - Give reasons why inductor is rarely used in large time constant applications.
  - State two applications of voltage comparators.
  - Draw the clamping circuit which can clamp negative peaks of input signal to above time axis.
  - State two applications of bi stable multivibrator.
  - 'Astable multivibrator can be used as square wave generator', justify your answer.
  - State any two methods of generating time base waveform.
  - State the factors influencing stability of relaxation dividers.
  - 'Logic gates are non-linear', justify your answer.
  - Define gain of sampling gate.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 (a) Discuss the response of High pass RC circuit with the help of waveforms: (i) Step Input. (ii) Ramp input.  
 (b) Explain how Low pass RC circuit will act as Integrator.

**OR**


- 3 (a) Discuss the response of Low pass RC circuit with the help of waveforms: (i) Step Input. (ii) Ramp input.  
 (b) Explain how High pass RC circuit will act as Differentiator.

**UNIT – II**

- 4 (a) State and prove clamping circuit theorem  
 (b) Draw a ideal clamping circuits for which output to satisfy following conditions:  
 (i) Positive peaks to be at zero level.  
 (ii) Negative peaks to be at zero level Assume sinusoidal input.

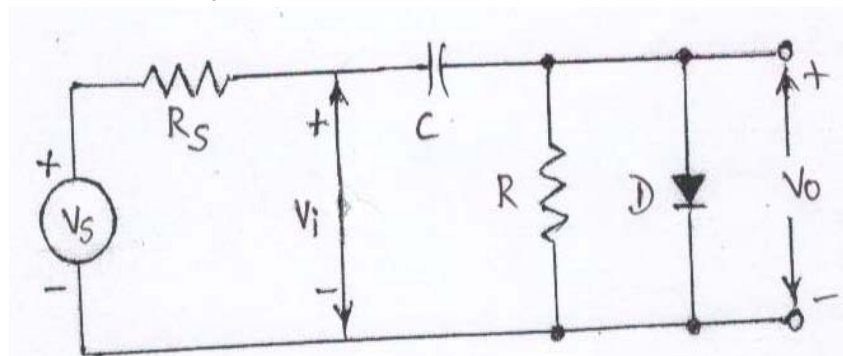**OR**


- 5 For the clamping circuit shown below, a symmetrical square wave is applied at  $t = 0$  with amplitude ranging from 0 to 10 volts and frequency of 5 kHz. Compute and sketch the output waveform for first several cycles. Given values are  $R_s = R_f = 100$  ohms,  $R = 10$  ohms and  $C = 1$   $\mu$ F.



Contd. in page 2

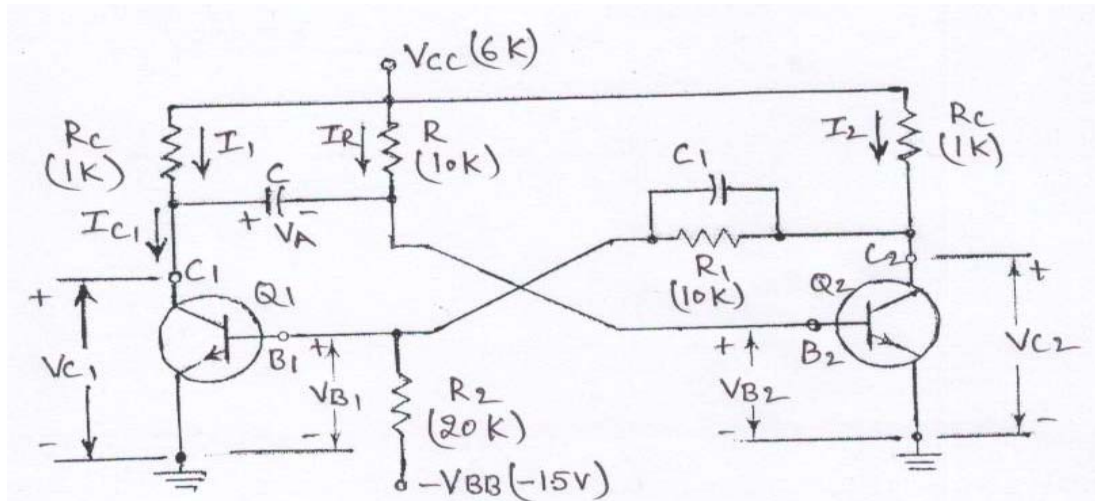
## UNIT - III

- 6 Compute the voltage levels of collector coupled monostable multivibrator at bases and collectors for the circuit shown below.



OR

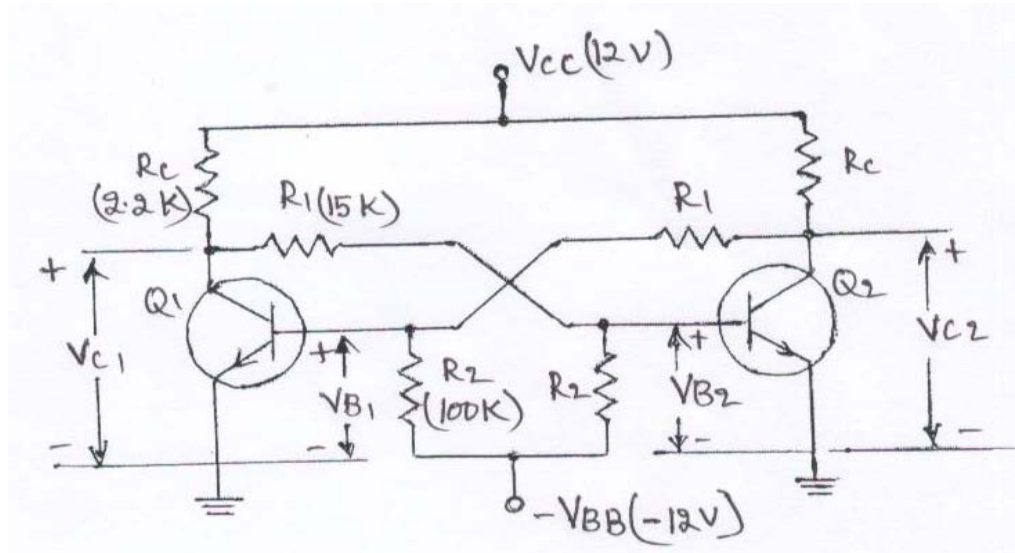- 7 Calculate the stable state currents and voltages for the bistable multivibrator circuit shown below. Assume that the transistors have a minimum  $h_{FE}$  value of 20.



## UNIT - IV

- 8 Explain the Millar sweep circuit. Also derive expressions for slope error and sweep speed.
- OR
- 9 With the help of block diagram and necessary waveforms, explain about stability of relaxation dividers.

## UNIT - V

- 10 Explain the bidirectional sampling gate using diodes. Derive the expression for gain.
- OR
- 11 Draw the circuits for OR gate using diodes for negative logic & positive logic and explain the operation.

\*\*\*\*\*