

B.Tech II Year II Semester (R13) Supplementary Examinations December 2016

PULSE & DIGITAL CIRCUITS

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- What is an attenuator? Explain the drawbacks of an uncompensated attenuator.
 - When does an RLC circuit function as a ringing circuit? What is the relation between quality factor Q and number of cycles N in the response of this circuit?
 - Discuss various diode clipping circuits that operate with two independent clipping levels.
 - Write the applications of voltage comparator.
 - Write the advantages of the d-c bistable multivibrator.
 - Draw the collector – coupled astable multivibrator circuit and sketch the wave forms.
 - Write the methods of linearity improvement. Draw the circuits for generating an impulse.
 - Define the terms Phase delay and Phase jitter.
 - Define the gain of the bidirectional diode gate.
 - Draw the block diagram of the sampling scope display.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 A 10 Hz symmetrical square wave whose peak-to-peak amplitude is 2 V is impressed up on a high-pass RC circuit whose lower 3dB frequency is 5 Hz. Calculate and sketch the output waveform for the first two cycles. What is the peak-to-peak output amplitude under steady-state conditions?

OR

- 3 Consider the response for an exponential input $V_i(t) = V(1 - e^{-t/\tau})$ applied to a high-pass RC circuit.

- (a) Derive the expression for $V_o(t)$ when $n \neq 1$ and when $n = 1$.

$$V_o(t) = \frac{V_n}{n-1} \left(e^{-x/n} - e^{-x} \right) \quad \text{if } n \neq 1$$

$$V_o(t) = Vx e^{-x} \quad \text{if } n = 1$$

- (b) Prove that the peak of the output pulse occurs at: $x = 2.30 \frac{n}{n-1} \log n$.

UNIT – II

- 4 (a) Discuss the various diode clipping circuits that operate with two independent clipping levels.
(b) Draw the circuit to obtain the pulse – type comparator output.

OR

- 5 (a) Draw Emitter coupled clipper circuit neatly and discuss in detail.
(b) Draw the typical diagram of clamping circuit taking source and diode resistances into account.

UNIT – III

- 6 (a) Draw a neat sketch of a fixed-bias n-p-n transistor bistable multivibrator.
(b) Calculate stable- state currents and voltages for the bistable multivibrator circuit consisting of two cross-coupled INVERTER circuits. Assume that the transistors have a minimum h_{FE} value of 20.

OR

- 7 (a) Draw the neat sketch of monostable multivibrator circuit.
(b) Design and calculate the Gate – width of a collector- coupled monostable multivibrator.

UNIT – IV

- 8 (a) Design a free-running UJT sweep waveform generator with the sweep amplitude of 6 volts. The sweep interval of a waveform is expected to be 3 msec with negligible retrace interval. The slope error $e_s = 0.75$. Determine the values of R_{b1} , R_{b2} , V_{BB} , V , R and C .
- (b) Write the Basic principle of Bootstrap time base generators.

OR

- 9 (a) State Synchronization in pulse wave generators.
- (b) Describe the pulse synchronization of relaxation devices with neat sketches.

UNIT – V

- 10 (a) Describe the unidirectional diode in detail. Also write the advantages.
- (b) Write the applications of sampling gates.

OR

- 11 (a) State AND, OR & NOT gates using diodes.
- (b) Write the comparisons between TTL and CMOS logic families.
