

B.Tech II Year II Semester (R13) Supplementary Examinations December 2016

ELECTRONIC CIRCUITS ANALYSIS & DESIGN

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- Define class AB amplifier.
 - Write the advantages of transformer coupling.
 - Calculate h_{fe} for short circuit current gain of transistor is 25 at a frequency of 2 MHz, if $f_{\beta} = 200 \text{ kHz}$.
 - An amplifier has a value of $R_{in} = 4.2 \text{ k}\Omega$, $A_v = 220$ and $\beta = 0.01$. Determine the value of input resistance of the feedback amplifier.
 - Write the advantages of negative feedback amplifier.
 - A wein-bridge oscillator has a frequency of 500 Hz, if the value of C is 100 pF, determine the value of R.
 - Describe the types of heat sinks.
 - Explain FET as voltage variable resistor.
 - What are the advantages of the double tuning?
 - Define the Q – factor in tuned circuits.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 Explain RC-coupled CE transistor stages. Show the middle and low frequency model for one stage. Write the expressions for current gains.

OR

- 3 With a neat diagram, analyze the complementary Darlington transistor.

UNIT – II

- 4 Derive the expression for CE short circuit current gain A_i as a function of frequency using hybrid – π model.

OR

- 5 Write a short note on gain bandwidth product of amplifier and derive the expression on the following:
- Product of voltage.
 - Product of current.

UNIT – III

- 6 What are the different types of negative feedback? Briefly explain how the input and output impedances of an amplifier are affected by the different types of negative feedback.

OR

- 7 Draw the circuit diagram of current shunt feedback and derive expressions for input and output resistances.

UNIT – IV

- 8 Draw the push pull power amplifier circuit. Derive the expression for the output current in push amplifier with base current as $I_b = I_{bn} \sin(\omega t)$.

OR

- 9 Explain the thermal run away, thermal resistance, thermal stability and thermal instability factors.

UNIT – V

- 10 Derive the expression for quality factor of a single tuned inductively coupled amplifier.

OR

- 11 What is the importance of stagger tuning? Explain briefly about stagger-tuned amplifier.