

B.Tech II Year II Semester (R13) Supplementary Examinations December 2016

**ANALOG ELECTRONIC CIRCUITS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- What are the different coupling schemes used in multistage amplifiers?
  - Write the expression for bandwidth of multistage amplifier.
  - What are the advantages of introducing negative feedback in amplifiers?
  - List the four basic feedback amplifier topologies.
  - What are the conditions for oscillation?
  - Define piezoelectric effect.
  - What are the merits of using push-pull configuration?
  - What is crossover distortion?
  - What is a clipper?
  - What are the important applications of Schmitt trigger circuit?

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 A multistage amplifier is to be constructed using four identical stages, each of which has a lower cut-off frequency of 15 Hz and upper cut-off frequency of 30 kHz.
- What will be the lower and upper cut-off frequencies of the multistage amplifier?
  - If the midband voltage gain of each stage is 8.2, what will be approximate gain of multistage amplifier at 7.5 kHz and at 300 kHz?

**OR**

- 3 What are cascaded amplifiers? Explain in detail the calculation of gain and bandwidth of single and multistage amplifiers.

**UNIT – II**

- 4 (a) The distortion in an amplifier is found to be 3%, when the feedback ratio of negative feedback amplifier is 0.04. When the feedback is removed, the distortion becomes 15%. Find the open and closed loop gain.
- (b) Explain the effect of negative feedback on amplifier characteristics.

**OR**

- 5 Draw the circuit diagram which has voltage series feedback and find its gain, input impedance and output impedance.

**UNIT – III**

- 6 Draw the circuit diagram of Hartley oscillator and explain its operation. Also derive the expression for frequency of oscillation.

**OR**

- 7 Explain how conditions for oscillations are satisfied for RC phase shift oscillator and derive its frequency of oscillation.

**UNIT – IV**

- 8 For a class B amplifier providing a 20 V peak signal to a 16 ohms load and a power supply of  $V_{cc} = 30$  volts. Determine input power, output power and efficiency.

**OR**

- 9 A complementary symmetry push-pull amplifier has capacitive load  $R_L = 8$  ohms, supply volt = 24 volts. Calculate  $(P_{ac})_{max}$ , power dissipation of each transistor and efficiency.

**UNIT – V**

- 10 Draw the circuit diagram of Astable multivibrator and derive the expression for on period and off period.

**OR**

- 11 Draw the circuit diagram of Schmitt trigger and explain its operation. Also derive the expressions of UTP and LTP.

\*\*\*\*\*