

**LINEAR & DIGITAL IC APPLICATIONS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- List the characteristics of an ideal op-amp.
  - Enlist the features of an instrumentation amplifier.
  - Draw the block diagram of PLL.
  - What is meant by Regenerative comparator?
  - What are the advantages of active filters over passive filters?
  - What are the different types of oscillators?
  - Give the classification of Integrated circuits.
  - Sketch the logic levels for typical CMOS logic circuits.
  - List the applications of multiplexers.
  - What is meant by Decade counter?

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 (a) Draw and explain the operation of op-amp based sample and hold circuit. And also draw the input and output waveforms.  
 (b) Define the following terms: (i) Slew Rate. (ii) Thermal drift.

**OR**

- 3 (a) Draw and explain the operation of instrumentation amplifier using transducer bridge.  
 (b) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 KHz.

**UNIT – II**

- 4 (a) Sketch the functional schematic of 555 timer and explain how it can be used as a monostable multivibrator. And also draw the waveforms.  
 (b) Calculate the values of the LSB and full scale output for an 8-bit DAC for the 0 to 10 V range.

**OR**

- 5 (a) Draw and explain the operation of counter type ADC.  
 (b) Define the following terms: (i) Resolution. (ii) Capture range.

**UNIT – III**

- 6 (a) Draw and explain the operation of op-amp based triangular waveform generator and also determine the frequency of triangular waveform.  
 (b) A first order low-pass Butterworth active filter has a cut-off frequency of 10 KHz and unity gain at low frequency. Find the voltage transfer function magnitude in dB, at 12 KHz for the filter.

**OR**

- 7 (a) With a neat sketch, explain the operation of Quadrature oscillator.  
 (b) If a band-pass filter has a lower cut-off frequency  $f_L = 250$  Hz and a higher cut-off frequency  $f_H = 2500$  Hz, then find its bandwidth and the resonant frequency.

**UNIT – IV**

- 8 (a) Give the comparison of various logic families.  
 (b) Draw and explain the operation of CMOS three-state buffer. And also draw its functional table.

**OR**

- 9 (a) Draw the circuit diagram of two-input LS-TTL NAND gate and explain its operation.  
 (b) Write a brief note on CMOS transmission gate.

**UNIT – V**

- 10 (a) Draw and explain the operation of 4-bit parallel binary adder/subtractor circuit.  
 (b) Convert a T flip-flop to D type flip-flop.

**OR**

- 11 (a) Design a code converter that converts BCD to excess-3 code.  
 (b) List the applications of shift registers.

\*\*\*\*\*