


B.Tech III Year I Semester (R13) Regular & Supplementary Examinations November/December 2016
LINEAR & DIGITAL IC APPLICATIONS
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
 (Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- What is an OPAMP?
 - What is the need of an instrumentation amplifier?
 - What is meant by PLL? Write any two applications of PLL.
 - What are the applications of an OP-AMP comparator?
 - List out important characteristics of digital IC's.
 - Classify the bipolar logic family by operation and give examples for each category.
 - What are the various steps in an HDL-based design flow?
 - Consider the circuit shown in Figure below, that saves the value of the input A into a register and then multiplies it with input C. Write the entity declaration that declares the interface signals for the circuit.

 

- What is a shift register?
- What is a PLD? Write the classification of PLDs?

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- List out ideal OP-AMP characteristics.
 - Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to 1 kHz.

OR

- What are the main features of IC 741 OP-AMP?
 - Design an inverting amplifier with an input resistance of 10 kΩ and gain of -5.

UNIT – II

- Design an astable multivibrator using an OP-AMP to generate a frequency of 1 kHz.
 - Draw the diode based log amplifier diagram and its output characteristics.

OR

- What is a Schmitt trigger? Draw the circuit of Schmitt trigger using 555 timer and explain its operation briefly.
 - What are the two basic modes in which the 555 timer operates? Briefly explain the differences between the two operating modes of 555 timer.

Contd. in page 2

UNIT – III

- 6 (a) Draw the CMOS 2-input AND gate circuit diagram and function table.
(b) Explain CMOS dynamic electrical behaviour in terms of transition time, propagation delay and power dissipation.

OR

- 7 (a) Explain the principle of a Emitter-Coupled Logic (ECL/CML) through Basic ECL inverter/buffer circuit with input HIGH and LOW.
(b) What are the advantages and disadvantages of ECL?

UNIT – IV

- 8 (a) Draw the VHDL programs file structure and explain the same with the syntax of a VHDL entity declaration and architecture definition.
(b) Explain structural, data flow and behavioral modelling styles using VHDL with suitable examples.

OR

- 9 (a) Write the syntax of a VHDL component declaration and by making use of component declaration, write a VHDL program for a prime-number detector.
(b) Write the syntax of a VHDL process statement and by making use of process statements, write a process-based dataflow VHDL architecture for the prime-number detector.

UNIT – V

- 10 Draw the logic symbol, truth table, logic diagram of a commercially available MSI 74 x 138 3-to-8 binary decoder and model the same using data flow-style VHDL program.

OR

- 11 Draw the traditional logic symbol, truth table, logic diagram of a standard MSI 74 x 194 4-bit, Universal Shift Register and model the same using data flow-style VHDL program.
