

B.Tech I Year II Semester (R15) Regular &amp; Supplementary Examinations May/June 2017

**NETWORK ANALYSIS**

(Common to ECE &amp; EIE)

Time: 3 hours

Max. Marks: 70

**PART – A**

(Compulsory Question)

\*\*\*\*\*


- 1 Answer the following: (10 X 02 = 20 Marks)
- Write short notes on source transformation.
  - State Kirchhoff's laws.
  - When an inductor is connected in a circuit, what is the status of inductor under steady state condition? Draw the equivalent circuit?
  - When a capacitor is connected in a circuit, what is the status of capacitor under steady state condition? Draw the equivalent circuit?
  - Define power factor and complex power.
  - Define impedance and apparent power.
  - What is the power factor in the series R-L-C circuit at resonance? What is the reason for that?
  - What is Q-factor?
  - Define hybrid parameters.
  - Draw constant-k low pass filter (proto type).

**PART – B**


(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 (a) State and explain Millman's theorem.  
 (b) By using Thevenin's theorem, determine the current through  $5\ \Omega$  resistor (All resistances are in  $\Omega$ ) as shown in figure.

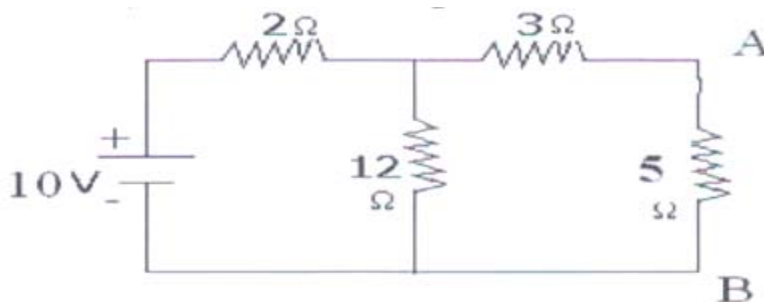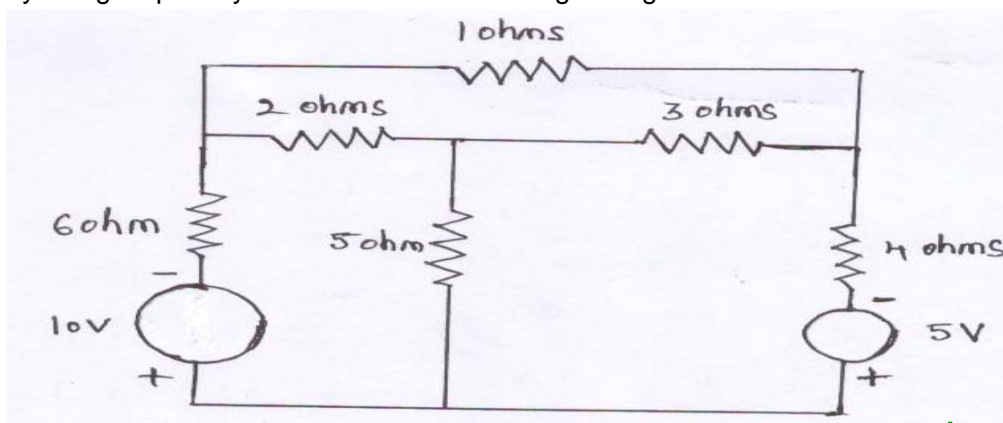
**OR**

- 3 (a) State and explain Maximum power transfer theorem.  
 (b) By using loop analysis find the current flowing through 5 ohms resistor.



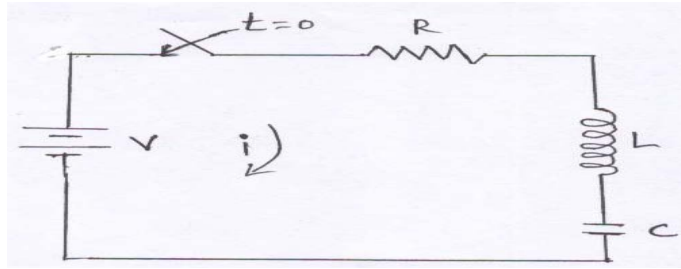
## UNIT - II

- 4 In the circuit shown below,  $V = 10\text{ V}$ ,  $R = 10\ \Omega$ ,  $L = 1\text{ H}$  and  $C = 10\ \mu\text{F}$ . The capacitor is initially uncharged. The switch is closed at  $t = 0$ . Determine  $i(0^+)$ ,  $\frac{di}{dt}(0^+)$  and  $\frac{d^2i}{dt^2}(0^+)$ . And also derive the formulae used.



OR

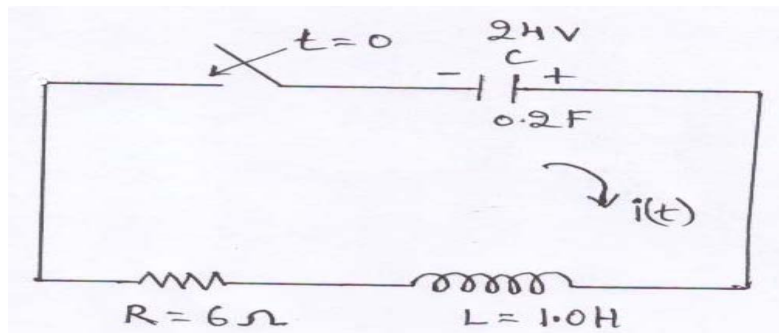- 5 In the circuit shown below,  $L = 1\text{ H}$ ,  $R = 6\ \Omega$  and  $C = 0.2\text{ F}$ . The capacitor is initially charged to  $24\text{ V}$  and the switch is closed at  $t = 0$ . Determine the expression for  $i(t)$  and the value of current at one second after the switch is closed. And also derive the formulae used.



## UNIT - III

- 6 (a) Show that the power dissipated by a pure, capacitor excited by a sinusoidal voltage source is zero.  
 (b) A series circuit consisting of a  $10\ \Omega$  resistor, a  $100\ \mu\text{F}$  capacitance and a  $10\text{ mH}$  inductance is driven by a  $50\text{ Hz}$  AC voltage source of maximum value  $100\text{ V}$ . Calculate the equivalent impedance, current in the circuit, the power factor and power dissipated in the circuit.

OR

- 7 (a) Derive the expression for instantaneous power when a series R-L circuit excited by a sinusoidal source.  
 (b) A series circuit to which  $100\text{ V}$  is applied, consists of a  $10\ \Omega$  resistance, a  $5\ \Omega$  condenser and a resistor  $R$  in which  $50\text{ watts}$  are lost and a reactance  $X_L$  which absorbed a reactive power of  $100\text{ VAR}$ . Calculate the values of  $R$  and  $X_L$  that satisfy the stated conditions.

## UNIT - IV

- 8 (a) Explain in detail about linear transformer.  
 (b) Show that  $Q_0 = \omega_0 L/R = f_0/BW$  for a series RLC circuit.

OR

- 9 (a) Show that the resonant frequency  $\omega_0$  of an RLC series circuit is the geometric mean of  $\omega_1$  and  $\omega_2$ , the lower and upper half power frequencies respectively.  
 (b) Given a series RLC circuit with  $R = 100\ \text{ohms}$ ,  $L = 0.5\text{ H}$  and  $C = 40\ \mu\text{F}$ . Calculate the resonant, lower and upper half - power frequencies.

## UNIT - V

- 10 (a) Define and explain short circuit parameters by taking one example.  
 (b) A low pass  $\pi$  section filter consists of an inductance of  $25\text{ mH}$  in the series arm and two capacitors of  $0.2\ \mu\text{F}$  in the shunt arms. Calculate the cut off frequency, design impedance, attenuation at  $5\text{ kHz}$  and phase shift at  $2\text{ kHz}$ . Also find the characteristic impedance at  $2\text{ kHz}$ .

OR

- 11 (a) Derive the relation between transmission and impedance parameters.  
 (b) A T-section low pass filter has an inductance of  $30\text{ mH}$  in each of the series arms and a shunt arm capacitance of  $0.25\ \mu\text{F}$ . Calculate the cut off frequency, characteristic impedance, ratio of input, output voltages and phase shift at: (i)  $1\text{ kHz}$ . (ii)  $5\text{ kHz}$ .