

ELECTRONIC DEVICES & CIRCUITS

(Common to EEE, ECE and EIE)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) Briefly write about diode resistance.
 - (b) Write major differences between zener breakdown and avalanche breakdown.
 - (c) Define TUF & PIV.
 - (d) Define & Classify filters.
 - (e) Briefly explain reach through effect.
 - (f) Draw the symbols for NPN (BJT), PNP (BJT), N-channel JFET and P-channel JFET.
 - (g) What is the importance of biasing?
 - (h) Write short notes on thermal runaway.
 - (i) Sketch the transistor hybrid model.
 - (j) Draw small signal model for FET.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) Derive diode current equation.
(b) A silicon diode has a saturation current of 7.5 μA at room temperature 300 K. Calculate the saturation current at 400 K.

OR

- 3 Explain construction and operation of UJT & SCR with necessary diagrams.

UNIT – II

- 4 Explain construction and operation of a bridge rectifier and derive its expressions.

OR

- 5 (a) Discuss full wave rectifier with L-section filter.
(b) Design a filter for full wave rectifier circuit with LC filter to provide an output voltage of 10 V with a load of 200 mA and the ripple is limited to 2%.

UNIT – III

- 6 Draw and explain characteristics of Common Collector configurations.

OR

- 7 Explain construction and operation of N-channel Enhancement & Depletion mode MOSFET.

UNIT – IV

- 8 Why self bias technique is so popular? And derive its three stability factors.

OR

- 9 What is the difference between bias stabilization & bias compensation? And also explain any two methods of bias compensation.

UNIT – V

- 10 Discuss generalized analysis of transistor amplifier model using h-parameters.

OR

- 11 Discuss generalized analysis of FET amplifier model using small signal model.