

B.Tech II Year II Semester (R15) Regular Examinations May/June 2017

SWITCHING THEORY & LOGIC DESIGN

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- Convert $(0.515)_{10}$ to octal.
 - What you mean by weighted code?
 - What are the universal gates? Why they are called universal gates?
 - Find the minterm expansion of $f(a, b, c, d) = a'(b' + d) + acd'$.
 - Explain binary subtractor.
 - What are the applications of multiplexers?
 - Write the differences between Latches and flip flops?
 - Draw the circuit of Johnsons counter.
 - Write the classification of semiconductor memories?
 - Give the comparison between ROM and PROM.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)**UNIT – I**

- 2 Why are complements used in binary arithmetic? What are the advantages and disadvantages of using 2s complement notation in binary arithmetic?

OR

- 3 Convert the following numbers as indicated:

- $(4350)_5 = ()_2$
- $(11010011)_2 = ()_{16}$
- $(552)_6 = ()_8$
- $(1001001.011)_2 = ()_{10}$
- $(2AC5.D)_{16} = ()_{10}$

UNIT – II

- 4 Simplify the following Boolean expressions to a minimum number of literals:

- $A'C' + ABC + AC'$.
- $(A' + C)(A' + C')(A + B + C'D)$.

OR

- 5 Simplify the following Boolean function to a minimum number of literals. $F(A, B, C) = \sum(1, 4, 5, 6, 7)$. Draw the Logic diagram using NAND gates.

UNIT – III

- 6 Design a 4-bit comparator using four 1-bit comparator modules.

OR

- 7 Implement 64 x 1 multiplexer with four 16 x 1 and one 4 x 1 multiplexer (use only block diagram).

UNIT – IV

- 8 Draw the logic diagram of a JK flip flop and using excitation table, explain its operation.

OR

- 9 Convert T-flip flop into D, JK and SR flip flop.

UNIT – V

- 10 Implement the following Boolean functions using a PAL that has four sections with three product terms each: $F_1(A, B, C, D) = \sum(2, 12, 13)$ and $F_2(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$.

OR

- 11 Given a 32 x 8 ROM chip with an enable input, show the external connection necessary to construct a 128 x 8 ROM with four chips and a decoder.
