

B.Tech III Year I Semester (R15) Supplementary Examinations June 2018
LINEAR & DIGITAL IC APPLICATIONS
 (Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
 (Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- When is an Op-Amp said to be an ideal?
 - Draw sample and hold circuit.
 - Draw the functional diagram of successive approximation ADC.
 - A 12 bit DAC has a resolution of 20m V/LSB. Find the full scale output voltage.
 - Find the order of a low pass Butterworth filter that is to provide 40dB attenuation at $\omega/\omega_h = 2$.
 - Design a phase shift oscillator to oscillate at 100Hz.
 - Mention the advantages of integrated circuits over discrete components.
 - What happens when excess gate voltage is given to CMOS devices?
 - Design a full adder circuit using decoder.
 - Design an 1-bit magnitude comparator.

PART – B
 (Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) Elaborate on an Op-Amp circuit which can generate single output pulse with adjustable time duration in response to a trigger signal.
 (b) Design an amplifier with a gain of -10 and input resistance equal to 10 k Ω .

OR

- 3 State the need for frequency compensation technique. With neat gain V_S frequency curves elaborate and derive the necessary equations used for different compensating techniques.

UNIT – II

- 4 What output voltage will be produced by a D/A converter whose output range is 0 to 10 V and whose input binary number is:
 (i) 10 (for 2-bit DAC)
 (ii) 0110 (for 4-bit DAC)
 (iii) 10111100 (for 8-bit DAC).

OR

- 5 Derive lock-in range and capture range of PLL with its neat block diagram and its explanation.

UNIT – III

- 6 (a) What are delay equalizers and why is it called so? With circuit diagram, derive the necessary equations to justify it.
 (b) Design a triangular wave generator using Op-Amp.

OR

- 7 Derive the output frequency of VCO.

UNIT – IV

- 8 Differentiate between MOS and CMOS. Elaborate on open drain and tristate CMOS outputs.

OR

- 9 Design a two input NAND gate using TTL open collector output and tristate output.

UNIT – V

- 10 Design a synchronous decade counter using D flip-flop.

OR

- 11 (a) Design a full subtractor circuit using 4x1 multiplexers.
 (b) Design a 2-bit magnitude comparator.
