

B.Tech II Year II Semester (R15) Regular Examinations May/June 2017
BASIC ELECTRICAL & ELECTRONICS ENGINEERING
 (Mechanical Engineering)


Time: 3 hours

Max. Marks: 70

Answer all the questions
 (Use single answer booklet only)

PART – A**UNIT – I**

- 1 (a) State the Kirchoff's voltage law and current law and explain with an example.
 (b) Find the total resistance between A&B terminals for the given network.

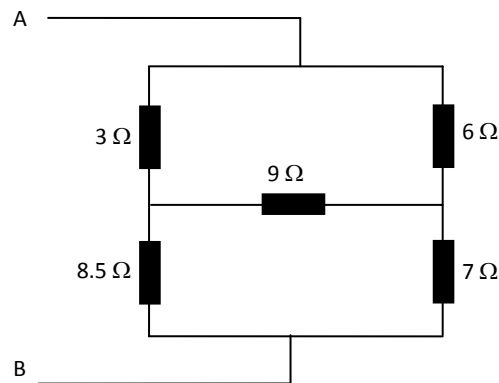**OR**

- 2 (a) State and explain Norton's theorem.
 (b) With suitable example, explain how the star connected network is transformed to delta.

UNIT – II

- 3 (a) Explain the applications of different types of D.C motors.
 (b) A 4-pole dc shunt generator having a field and armature resistance of 100 Ω and 0.2 Ω respectively supplies parallel connected 100 number of 200 V, 40 W lamps. Calculate the armature currents and generated emf. Allow 1 V per brush contact drop.

OR

- 4 (a) With neat sketches, explain how the DC Generators are classified.
 (b) A 500 V shunt motor runs at its normal speed of 250 rpm when the armature current is 200 A. The resistance of armature is 0.12 Ω. Calculate the speed when a resistance is inserted in the field reducing the shunt field to 80% of normal value, and the armature current is 100 A.

UNIT – III

- 5 (a) Derive an expression for the induced emf of a transformer.
 (b) A 3-phase, 6-pole, 50 Hz induction motor has a slip of 1% at no load and 3% at full load. Find:
 (i) No load speed. (ii) Full load speed. (iii) Frequency of rotor current on full load.

OR

- 6 (a) Explain the principle and operation of three phase induction motors.
 (b) The maximum flux density in the core of 250/3000 V, 50 Hz, 1-phase transformer is 1.2 Wb/m². If the emf per turn is 8 V, determine: (i) Primary and secondary turns. (ii) Area of the core.

Contd. in page 2

PART – B

UNIT – I

7 Draw the circuit diagram of FWBR and explain its operation with the help of input and output waveforms and derive the ripple factor.

OR

8 Draw VI characteristics of PN junction diode and the reverse saturation current of a Silicon PN junction diode is $10 \mu A$. Calculate the diode current for the forward bias voltage of 0.6 V at room temperature.

UNIT – II

9 Explain the input and output characteristics of a common collector transistor configuration.

OR

10 A transistor has $I_b=100 \mu A$ and $I_C = 2 \text{ mA}$, find: α, β, I_e and if I_b changes by $+25 \mu A$ and I_C changes by 0.6 mA , then find the new value of β .

UNIT – III

11 What is the function of oscillator? How the various oscillators are classified? Explain about LC tuned type of oscillators.

OR

12 Explain about inverting and non-inverting op-amps.
