



C20-AEI-106

7013

BOARD DIPLOMA EXAMINATION, (C-20)

OCTOBER / NOVEMBER—2023

DAEIE – FIRST YEAR EXAMINATION

BASIC ELECTRICAL ENGINEERING

Time : 3 Hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.


1. Define loop and branch in circuit.
2. List any three differences between active and passive circuits.
3. Define resonance in series circuit.
4. Write the formula of Impedance and power in RLC series circuit.
5. List any three electrical appliances of heat produced due to electric current in metal.
6. A transformer has 8 windings in its primary core and 5 in its secondary core. If the primary voltage is 240 V then, find the secondary voltage.
7. Define regulation of transformer.
8. State the losses in a transformer.
9. Classify DC machines with reference to excitation.
10. State Fleming's right hand rule.

PART—B

8×5=40

- Instructions :** (1) Answer either (a) or (b) from each questions.
(2) Each question carries **eight** marks.
(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

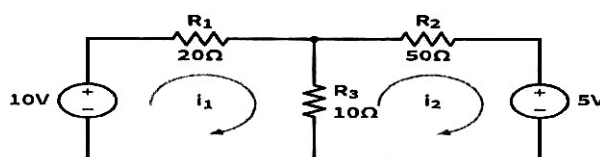11. (a) Find the current flowing through $10\ \Omega$ resistor by using Kirchhoff's laws.



(OR)

- (b) Explain star and delta circuits.

12. (a) Derive the relationship between voltage and current in pure inductive circuit.

(OR)

- (b) Differentiate between series and parallel resonances in any four aspects.

13. (a) Explain the construction and working of Electric Kettle.

(OR)

- (b) Explain the construction and working of Geyser.

14. (a) Explain the working principle of current transformer.

(OR)

- (b) Explain the working principle of Isolation transformer.

15. (a) Explain the construction of DC generator.

(OR)

- (b) Explain the principle of Alternator.

PART—C

10×1=10

- Instructions :** (1) Answer the following question.
(2) The question carries **ten** marks.
(3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

16. Derive equation for the resonant frequency in RLC parallel circuit.

★★★