



**C20-BM-304**

**7222**

**BOARD DIPLOMA EXAMINATION, (C-20)  
OCTOBER/NOVEMBER—2023**

**DBME - THIRD SEMESTER EXAMINATION**

**DIGITAL ELECTRONICS**

*Time : 3 Hours ]*

*[ Total Marks : 80*

---

**PART—A**

**3×10=30**

- Instructions :** (1) Answer **all** questions.  
(2) Each question carries **three** marks.  
(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. State De-Morgan's theorem.
2. Define the truth tables of NAND and NOR gates.
3. Draw half-adder circuit using an Ex-or gate.
4. Compare serial adder with parallel adder.
5. Construct full adder using 3x8 decoder.
6. Define edge triggering in flip-flops.
7. Write the use of shift registers as memory.
8. State any three applications of counters.
9. Define word length and access time.
10. Classify different types of memories.

**PART—B**

8×5=40

- Instructions :** (1) Answer **all** questions.  
(2) Each question carries **eight** marks.  
(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

**11.** (a) Draw an open collector TTL NAND gate and explain its working.

**(OR)**

(b) Compare the performance of TTL gate with respect to CMOS gate.

**12.** (a) Explain 4-bit parallel adder and 2's compliment subtractor with circuit.

**(OR)**

(b) Compare serial adder with parallel adder and design a 4 to 2 line priority encoder.

**13.** (a) Explain the working of a RS-flip-flop with truth table.

**(OR)**

(b) Explain the working of NAND/NOR gate latch.

**14.** (a) Explain the circuit of a decade counter with wave form and truth table.

**(OR)**

(b) Draw the 4-bit ring counter circuit and explain its operation.

**15.** (a) Explain the concept of touch screen display and list the advantages of LED display with LCD display.

**(OR)**

(b) Compare the advantages and disadvantages of dynamic RAM over static RAM.

**PART—C**

10×1=10

- Instructions :** (1) Answer the following question.  
(2) The question carries **ten** marks.  
(3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 16.** Can the selection of JK flip-flop in digital circuits be replaced with RS flip-flop? Justify your answer.

★★★