

# **7613**

## **BOARD DIPLOMA EXAMINATION, (C-20)**

## OCTOBER / NOVEMBER—2023

#### **DBME - FIFTH SEMESTER EXAMINATION**

MEASUREMENT AND TEST EQUIPMENT

Time: 3 Hours [ Total Marks: 80

#### PART—A

 $3 \times 10 = 30$ 

**Instructions:** (1) Answer **all** questions.

- (2) Each question carries **three** marks.
- (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.
- **1.** Classify the methods of measurement with examples.
- **2.** List the precautions to be taken while using an ammeter.
- **3.** List the applications of Maxwell's bridge.
- **4.** Write the advantages of digital instruments over analog instruments.
- **5.** Define the term Resolution.
- **6.** Draw the block diagram of CRO.
- **7.** List the condition for stationary waveform.
- **8.** State the principle of energy measurement.
- **9.** List the applications of logic probes.
- **10.** State the necessity of Recorder.

**PART—B** 8×5=40

**Instructions:** (1) Answer **all** questions.

- (2) Each question carries eight marks.
- (3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.
- **11.** (a) Explain the characteristics of (i) repeatability, (ii) resolution and (iii) sensitivity.

(OR)

- (b) Explain the principle characteristics of (i) back slash, (ii) dead zone and (iii) hysteresis.
- **12.** (a) Explain the construction and working principle of series type ohmmeter.

(OR)

- (b) Explain inductance measurement using Maxwell bridge.
- **13.** (a) Explain the ramp type digital voltmeter with block diagram.

(OR)

- (b) Explain the working of digital LCR meter with block diagram.
- **14.** (a) Draw CRT and describe the functions of different parts.

(OR)

- (b) Explain the horizontal deflection system.
- **15.** (a) Explain the working of AF power meter.

(OR)

(b) Explain the methods of testing active components.

/7613 2 [ Contd...

**Instructions:** (1) Answer the following question.

- (2) The question carries **ten** marks.
- (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.
- **16.** Explain the working of digital multimeter with block diagram and list its specifications.

