



C20-CM-302

7235

**BOARD DIPLOMA EXAMINATION, (C-20)
OCTOBER/NOVEMBER—2024
DCME – THIRD SEMESTER EXAMINATION
DIGITAL ELECTRONICS**

Time : 3 Hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. Convert $(42.5)_{10}$ into binary.
2. Give the table showing hexadecimal digits from 0 to 15 and its binary values.
3. State de-Morgan's theorem.
4. Give the EX-OR gate logic symbol with truth table.
5. Define positive and negative logic levels.
6. Define triggering.
7. List the types of counters.
8. State the need of a register.
9. Define the term decoder.
10. List the applications of multiplexer.

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **eight** marks.
(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

11. (a) Convert $(10101110)_2$ into decimal and $(10100110)_2$ into hexadecimal.

(OR)

(b) Draw and explain the Excess-3 codes with BCD codes in a table and explain one example.

12. (a) Simplify the Boolean expression $Y = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C$ using k-map method to their minimum sum of products form and realize using basic gates.

(OR)

(b) Construct full adder using two half adders and an OR gate.

13. (a) Explain the working of NAND latch circuit with truth table and timing diagram.

(OR)

(b) Explain with block diagram and truth tables the working of D-flip-flop.

14. (a) Draw and explain module-16 ripple counter circuit diagram with truth table.

(OR)

(b) Explain the working of universal shift register.

15. (a) Draw and explain the operation of 1×4 de-multiplexer circuit diagram with truth table.

(OR)

(b) Explain programmable logic array (PLA).

PART—C

10×1=10

- Instructions :** (1) Answer the following question.
(2) The question carries **ten** marks.
(3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 16.** Explain the working of functional difference between up/down Counter and up/down asynchronous counter with a circuit diagram.

★★★