

Code No: 113AU

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech II Year I Semester Examinations, April/May - 2018****ELECTRONIC DEVICES AND CIRCUITS****(Common to EEE, ECE, CSE, EIE, IT, MCT)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Define static resistance. [2]
- b) Write the effect of temperature on diode characteristics. [3]
- c) What is regulation? [2]
- d) List the differences between different filters. [3]
- e) Define current amplification factor. [2]
- f) What is emitter follower? Draw the circuit diagram of CC configuration. [3]
- g) What is the need of biasing? [2]
- h) Explain, how to avoid thermal runaway? [3]
- i) Mention the applications of FET. [2]
- j) Why the input impedance of FET is higher than BJT? [3]

PART-B**(50 Marks)**

- 2.a) Draw and explain V-I characteristics of PN diode.
 - b) With suitable expressions explain transition capacitance. [5+5]
- OR**
- 3.a) Describe the principle of operation of tunnel diode.
 - b) Explain the working of semiconductor photo diode. [5+5]
- 4.a) Derive the equation for ripple factor of half wave rectifier with C-filter.
 - b) With suitable wave forms explain bridge rectifier. [5+5]
- OR**
- 5.a) Describe the operation of full wave rectifier with π -section filter.
 - b) A 50 Hz transformer having 60 V r. m. s. on each side of the centre tap supplies a full wave rectifier circuit. The circuit load is 210Ω with a shunt capacitor filter of $1000 \mu\text{F}$. Find the ripple factor. [5+5]
- 6.a) Explain the working of PNP transistor.
 - b) Write the differences between CB, CE, and CC Amplifier Configurations. [5+5]
- OR**
- 7.a) Derive the relation between α and β .
 - b) Discuss, how the h-parameters are determined from transistor Characteristics. [4+6]

- 8.a) Derive the equation for stability factor for fixed bias.
b) Draw and explain the circuit for bias compensation using diode. [5+5]

OR

- 9.a) Write a short note on Stabilization against variations in V_{BE} and β .
b) For the transistor amplifier circuit, when signal changes by 0.012 V, the base current changes by 9 μA and collector current by 1.3 mA. If the collector load $R_C = 6 \text{ K}\Omega$, $R_L = 12 \text{ K}\Omega$. Determine input resistance, current gain and voltage gain. [5+5]

- 10.a) Write short notes on Small Signal Model of JFET.
b) Draw and explain drain and transfer characteristics of depletion type MOSFET. [5+5]

OR

- 11.a) With neat sketch, discuss about common source FET amplifier.
b) Explain, how FET is working as Voltage Variable Resistor? [6+4]

---ooOoo---