

Code No: 113BR

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, February/March-2016

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.


Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**


- 1.a) Explain the basic circuit components. [2]
- b) Explain Kirchoff's laws. [3]
- c) What is meant by power factor? [2]
- d) Derive an expression for average power across a capacitor connected to an alternating supply. [3]
- e) Give the constructional details of a 1- ϕ transformer. [2]
- f) Define regulation of a Transformer. [3]
- g) What is the condition for maximum efficiency of a d.c machine? [2]
- h) Define slip and slip speed of a 3- ϕ Induction motor. [3]
- i) What are the materials with which pointer and scale are manufactured? [2]
- j) What are the advantages and disadvantages of M.I instrument? [3]

PART-B**(50 Marks)**

- 2.a) State and explain Thevenin's theorem.
- b) Determine the current I in the network by using Thevenin's theorem (Figure 1). [4+6]

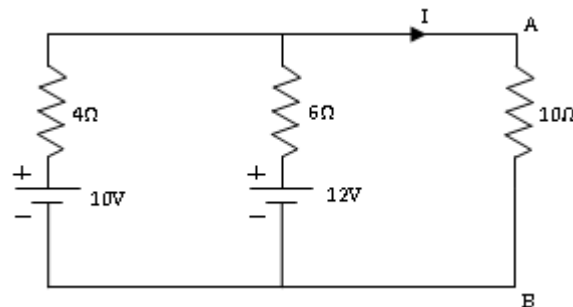**Figure: 1****OR**

- 3.a) State and explain Max. Power transfer theorem.
- b) Calculate the current flowing through $R_L = 20\Omega$ of the network shown in the figure 2 by using Thevenin's theorem. [4+6]

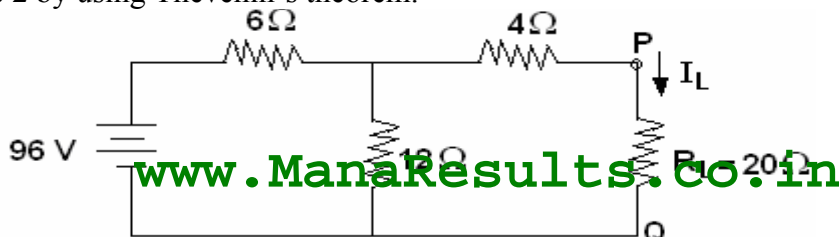**Figure: 2**

4. A $20\ \Omega$ resistance and 30mH inductance are connected in series and the circuit is fed from a 230V , 50Hz , AC supply. Find
- Reactance across the inductance, impedance, admittance, current.
 - Voltage across the resistance.
 - Voltage across the inductance.
 - Reactive and Active powers.
 - Power Factor. [2+2+2+2+2]

OR

5. Explain the behaviour of AC through:
- Pure R
 - Pure L
 - Pure C circuits.
- For each case, derive the instantaneous value of V and I , Impedance, Average power, Power factor, Instantaneous power and the relevant phasors. [3+3+4]

- With the help of diagram explain the principle of operation of transformer.
- Derive an expression for emf induced in a transformer. [5+5]

OR

- Determine the efficiency of a $150\ \text{KVA}$ transformer at 50% full load and 0.8 power factor lag if the copper loss at full load is 1600 watts and iron loss is 1400 watts.
- Draw the no load and full load phasor diagrams of a transformer. [5+5]

- Explain the principle of operation of $3\text{-}\phi$ induction machine with neat diagram.
- A 6 pole induction motor is fed from $60\ \text{Hz}$ supply. If the frequency of rotor EMF at full load is $2\ \text{Hz}$. Find the full load speed and %slip. [7+3]

OR

- With neat sketches, explain the construction and functions of the various parts of a d.c. machine.
- A 100V series motor takes $45\ \text{A}$ when running at $750\ \text{rpm}$. Its armature resistance is $0.22\ \text{ohms}$, while the series field resistance is $0.13\ \text{ohms}$. Iron and frictional losses amounts to $750\ \text{W}$. Find the shaft power. [6+4]

10. Explain the following with reference to the measuring instruments:
- Deflecting torque
 - Controlling torque and
 - Damping torque. [3+3+4]

OR

11. Explain with neat sketch the construction and working of a PMMC. [10]

---ooOoo---