

R16

Code No: 133AJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, November/December - 2017****DIGITAL LOGIC DESIGN****(Common to CSE, IT)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Subtract the following using 1's and 2's complement $(101)_2 - (10110)_2$. [2]
- b) Distinguish between canonical and standard forms by giving an example. [3]
- c) Derive the sum of minterms for the function $f(a,b,c)=a'b+b'c'$ [2]
- d) Implement the following function using only NAND Gates $F=a.(b'+c')+(b.c)$. [3]
- e) Differentiate multiplexer and de-multiplexer. [2]
- f) Draw the diagram of 4-Bit Parallel adder cum parallel subtractor. [3]
- g) Show the excitation table and truth table of JK flip flop. [2]
- h) Differentiate critical and non-critical race. [3]
- i) Define Register Transfer Language. [2]
- j) Differentiate PLA and PAL. [3]

PART-B**(50 Marks)**

- 2.a) What are the various logic gates, give the representation along with the truth table.
- b) What is the use of complements? Perform subtraction using 7's complement for the given Base-7 numbers $(565)-(666)$. [5+5]

OR

- 3.a) Convert the following to the corresponding bases
 - i) $(9BCD)_{16} = (\quad)_8$
 - ii) $(323)_4 = (\quad)_5$
 - b) Given the 8 bit data word 11011011, generate the 12 bit composite word for the Hamming code that corrects and detects single errors. [5+5]
- 4.a) Derive the product of maxterms for $f(a,b,c,d)=a.b.c+ b'.d+c.d'$.
 - b) Derive and Implement Exclusive OR function involving three variables using only NAND function. [5+5]

OR

- 5.a) Obtain the simplified expression in SOP form of $F(a,b,c,d,e)=\sum(1,2,4,7,12,14,15,24,27,29,30,31)$ using K-maps.
- b) Implement the function $f(a,b,c)=\pi(0,1,3,4)$ using NAND-NAND two level gate structure. [5+5]

- 6.a) Implement an odd parity generator for 3-bit using a decoder.
b) Design a circuit for 2-bit binary multiplier. [5+5]

OR

- 7.a) Define a multiplexer? Draw a 4:1 multiplexer for the function
 $f(a,b,c,d)=\sum(0, 4,5,10,11,12,15)$
b) Design a full binary adder with two half adders and an OR gate. [5+5]

- 8.a) Explain about a NOR Latch in detail, with a neat diagram.
b) Design a 3-bit counter using T flip flops. [5+5]

OR

9. Define essential hazard? Implement SR Latch by avoiding Hazard. Neatly draw the diagram of SR latch before hazard and after Hazard elimination. [10]

10. Explain about RAM in detail. [10]

OR

11. What is a micro operation? List and explain its categories with relevant examples. [10]

---oo0oo---