

Code No: 152AP

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech I Year II Semester Examinations, August - 2019

BASIC ELECTRICAL ENGINEERING

(Common to EEE, CSE, IT)

Time: 3 hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART- A

(25 Marks)

- 1.a) What is the relationship between voltage and current in a capacitor? [2]
- b) What is reactive power? [2]
- c) What is magnetizing inductance? [2]
- d) What is the value of slip at rated speed? [2]
- e) What is an MCB? [2]
- f) What are the properties of ideal voltage source? [3]
- g) What is phasor? What is its significance? [3]
- h) How to improve the efficiency of transformer? [3]
- i) What is the operational difference between single phase and three phase induction motors? [3]
- j) How an ELCB works? [3]

PART-B

(50 Marks)

- 2.a) What is steady state response?
- b) How do you find out thevenin's resistance?
- c) Find the current 'i' in the circuit below figure 1. [3+3+4]

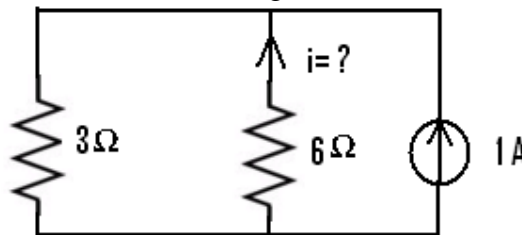


Figure: 1

OR

- 3.a) What is time constant of R-L circuit? What is its significance?
- b) What is the procedure to find out norton's current?
- c) Find the voltage 'V' in the circuit below figure 2. [3+3+4]

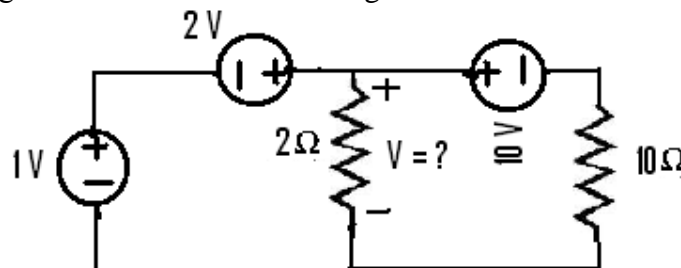


Figure: 2

- 4.a) How to represent two sinusoidal quantities with different phase angles as phasors?
- b) How RYB phase sequence is different from RBY phase sequence?
- c) What is the source impedance of the circuit below figure 3 if the AC source is replaced with DC source? [3+3+4]

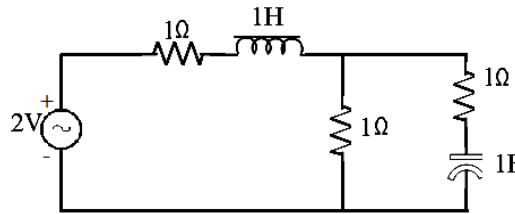


Figure: 3

OR

- 5.a) What is the significance of lagging power factor? How to understand?
- b) Where do we need star connected three phase systems?
- c) Find the currents represented in the circuit below shown in figure 4 at resonance. [3+3+4]

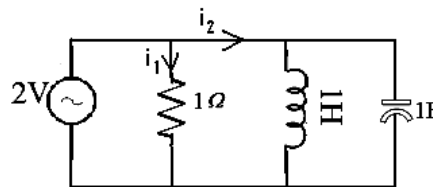


Figure: 4

- 6.a) What are the properties of an ideal transformer?
- b) What are the various connections of three phase transformer?
- c) A load of 10 kVA at 1100 V and unity power factor is to be supplied from a 2200 V source by means of an auto-transformer. Find the percentage of the volume of copper saved to two winding transformer of the same duty [3+3+4]

OR

- 7.a) How to represent leakage flux in equivalent circuit?
- b) What is the meaning of zero regulation in transformer?
- c) How the transformer behaves at no load? [3+3+4]

- 8.a) How a synchronous generator works?
- b) How the torque-slip characteristics vary with the variation in input voltage of induction motor?
- c) What are the limitations of DOL starting? [3+3+4]

OR

- 9.a) What is the constructional difference between synchronous and induction machine?
- b) How the torque-slip characteristics vary with the variation in rotor resistance of induction motor?
- c) How to increase of the speed of induction motor? [3+3+4]

- 10.a) How an MCB works?
- b) Why do we do Earthing?
- c) Explain various types of wires. [3+3+4]

OR

- 11.a) Draw the various characteristics of batteries.
- b) How to improve the power factor?
- c) Write short notes on battery backup. [3+3+4]