Code No: G6806/R13

M. Tech. I Semester Supplementary Examinations, January-2017

DIGITAL SYSTEM DESIGN

(Common to VLSI & ES, ES & VLSI, VLSID & ES, ES & VLSID, VLSI, VLSID, VLSISD, VLSI&ME, ES, DE&CS, E&CE and DECE)

Time: 3 hours

Max. Marks: 60

	Answer any FIVE Questions All Ouestions Carry Equal Marks								
1.	a	List out the cube based operations that can be used in cube based minimization algorithm and explain them with an example each.	6M						
	b	Apply CAMP algorithm to minimize the given 4 variable Boolean function $f(a, b, c, d) = \sum m (1, 3, 5, 7, 9, 10, 13, 14, 15)$	6M						
2.	a	Implement the following Boolean functions using PLA E1 (X, X, Z) = $\sum (1, 2, 4, 6)$ E2 (X, X, Z) = $\sum (0, 1, 6, 7)$ E3 (X, X, Z) = $\sum (2, 6)$	6M						
	b	List out the steps to be consider for PLA folding algorithm?	6M						
3.	a	Design a combinational circuit using a ROM. The circuit accepts a 3 bit number and generates an output binary number equal to the square of the input number.	8M						
	b	How a sequential circuit can be designed using FPGA?	4M						
4.	a	Using the path-sensitization method and Boolean difference method find the test vectors for SA0 fault on input line 1 and SA1 fault on the internal line 2 of the circuit shown in figure	8M						



b Write a short note on Fault classes and Models?

4M

1 of 2

WWW.MANARESULTS.CO.IN

Code No: G6806/R13

5.	a	Ps	Ns, z x=0, x=1	Conduct a Homing experiment and determine shortest homing sequence which identifies the final state of the given	8M		
		Α	B,0 D,0	state machine.			
		В	A,0 B,0				
		С	D,1 A,0				
		D	D,1 C,0				
					4M		
	b Explain the properties of a successor tree.						
6.	a	Simplify the Boolean expression using k-map $F = \pi M (0, 1, 3, 5, 6, 7, 10, 14, 15)$					
	b	Compare PROM, PLA and PAL.					
7.	a	Discuss the BIST scheme for PLD and CPLDs.					
	b	Classify the fault detection experiments for the sequential circuits with examples. 6					

Draw an ASM chart to design control logic of a binary multiplier. Realize the same using MUX, decoder and D-type flip flops. 8. 12M

WWW.MANARESULTS.CO.IN