

Code No: I6803/R16

M. Tech. I Semester Supplementary Examinations, February -2020

**CMOS ANALOG IC DESIGN**

Common to VLSI&ES (68), ES&VLSI (48), VLSID &ES (77), ES &VLSID (81), VLSI (57),  
VLSID (72), VLSI System Design (61) and VLSI & Micro Electronics (76)

Time: 3 Hours

Max. Marks: 60

---

*Answer any FIVE Questions  
All Questions Carry Equal Marks*

---

- |      |   |    |
|------|---|----|
| 1. a | Explain the various model parameters in MOS.  | 6M |
| b    | Discuss about the computer simulation models  | 6M |
| 2. a | Using small signal analysis, Derive an expression for the output resistance of the cascode current source | 6M |
| b    | Explain about the current mirror with degeneration helper with equations                                  | 6M |
| 3. a | Explain class A output amplifier.   | 6M |
| b    | With derivation explain the operation of single ended input current amplifier.                            | 6M |
| 4. a | Explain the procedure for the design of an op-amp.  | 6M |
| b    | Derive an expression for slew rate of a cmos op-amp.  | 6M |
| 5. a | Explain the circuit of a switched capacitor comparator.   | 6M |
| b    | Explain the operation of push-pull output comparator.   | 6M |
| 6. a | Explain any two of the op-amp compensation techniques.  | 6M |
| b    | Define and derive an expression for threshold voltage of a MOS.   | 6M |
| 7. a | With necessary circuit explain the current and voltage references.  | 6M |
| b    | Explain the operation of MOS switch.  | 6M |
| 8.   | Write short notes on the following  |    |
| a    | Open loop comparator  | 6M |
| b    | Cascode Op-amp  | 6M |

\*\*\*\*\*

1 of 1