

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[4957]-1033

S.E. (Electrical) (First Semester) EXAMINATION, 2016

ANALOG AND DIGITAL ELECTRONICS

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Attempt Q. Nos. 1 or 2, Q. Nos. 3 or 4, Q. Nos. 5 or 6, Q. Nos. 7 or 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Assume suitable data, if necessary.

(v) Use of non programmable calculator is permitted.

1. (a) Design and explain the operation of MOD 10 asynchronous counter with related timing diagram. [6]

(b) Convert the number into its equivalent number with appropriate step. [6]

(i) $(0.6234)_{10} = (\quad)_8$

(ii) $(B65F)_{16} = (\quad)_{10}$.

Or

2. (a) Draw circuit and explain 4 bit universal shift register. [6]

(b) Minimize the following Boolean expression using K-map and realize it using the basic gates. $Y = \sum m(1, 3, 5, 9, 11, 13)$. [6]

P.T.O.

3. (a) Explain the difference between fixed and variable regulator. Explain with suitable circuit diagram, how IC-317 can act a variable voltage regulator. Also derive formula for variable voltage available at the output of IC LM 317 in terms of circuit parameters. [7]
- (b) Draw the diagram of IC 555 configured in Astable mode. Draw necessary waveforms. Give the formula for T_{on} and T_{off} . [6]

Or

4. (a) Explain the application of OPAMP as Schmitt Trigger. Comment on hysteresis. [7]
- (b) Explain first order low pass filter with neat circuit diagram and frequency response. [6]
5. (a) Draw and explain transfer characteristics of JFET. [6]
- (b) Explain the operation transistorized transformer coupled CE amplifier with neat circuit diagram. [7]

Or

6. (a) What is DC load line ? Derive equation for DC load line and show Q point on DC load line. [6]
- (b) Write a short note on push pull amplifier. [6]
7. (a) A single phase full bridge diode rectifier is supplied from 230 V, 50Hz source. The load consist of $R = 10\Omega$ and a large inductance so as to render the load current constant. Determine :
- (i) Average values of output voltage and current. [6]
- (ii) Average and rms values of diode currents.
- (b) Explain the working of single phase full wave bridge rectifier with RL load with neat sketch and draw its input and output waveform. [7]

Or

8. (a) What are the advantages and disadvantages of three phase rectifier over single phase rectifier. [7]
- (b) The single phase half wave rectifier has purely with R load. Determine : [6]
- (i) Efficiency
 - (ii) Form factor
 - (iii) Ripple factor
 - (iv) Transformer utilization factor
 - (v) Peak inverse voltage.