

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5152]-144

S.E. (Electrical) (I Sem.) EXAMINATION, 2017

ANALOG AND DIGITAL ELECTRONICS

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B. :—** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.
(ii) Neat diagrams must be drawn wherever necessary.
(iii) Figures to the right indicate full marks.
(iv) Assume suitable data, if necessary.
(v) Use of non-programmable calculator is allowed.

- 1.** (a) Perform the following arithmetic operations Convert : [6]
(i) $(623.77)_8 = ()_{10}$
(ii) $(2ACF.D)_{16} = ()_8$
(b) Write short notes on : [6]
(i) Gray code and its binary conversion
(ii) Excess-3 code

Or

- 2.** (a) Explain the working of serial input serial output shift (SISO) register with a neat circuit diagram. [6]
(b) Explain the working of Master–Slave JK flip-flop. [6]

P.T.O.

3. (a) Explain the function of 78XXX and 79XX voltage regulator. [6]
- (b) Explain OP AMP as a V-I & I-V converter. [7]

Or

4. (a) Compare open loop & closed loop configuration of OP-AMP. [6]
- (b) Draw neat diagram & explain operation of OP-AMP as square wave generator with waveforms. [7]
5. (a) Write a short note on Darlington pair. [6]
- (b) Define important parameters of JFET. [7]

Or

6. (a) Write short note on Push Pull amplifier with waveforms. [7]
- (b) Draw and explain RC coupled amplifier with frequency response. [6]
7. (a) Explain the working of single phase full wave bridge rectifier with R load and draw its output voltage and current waveforms. [6]
- (b) Why filters are required ? Explain LC Filter. [6]

Or

8. (a) Explain working of three phase full wave bridge rectifier with R load. [6]
- (b) A half wave rectifier employs a diode having forward resistance of 10 ohm. If input voltage to the rectifier circuit is 12 V rms, find the dc output voltage at a load of 100 mA and PIV. [6]