

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[4857]-1033

S.E. (Electrical) (First Semester) EXAMINATION, 2015
ANALOG AND DIGITAL ELECTRONICS
(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B. :—** (i) Neat diagrams must be drawn wherever necessary.
(ii) All questions are compulsory i.e. (Solve Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6 and Q. No. 7 or Q. No. 8).
(iii) Assume suitable data, if necessary.
(iv) Use of logarithmic tables, slide rule, Mollier charts, pocket calculator and steam table is allowed.
(v) Figures to the right indicate full marks.

- 1.** (a) Convert the following numbers : [6]
(i) $(754.51)_7$ to hexadecimal
(ii) $(7BC.A3)_{16}$ to decimal
(iii) Binary equivalent 110011001010 into its gray code.
(b) Design MOD-5 synchronous up counter using JK flip-flop. [6]

Or

- 2.** (a) Draw and explain 4-bit SISO shift register. [6]
(b) Draw the diagram, timing diagram and write the truth table for twisted ring counter. [6]
- 3.** (a) Explain the fixed voltage regulator IC. [6]
(b) Explain the working of op-amp as ZCD with waveforms.[7]

P.T.O.

Or

4. (a) Explain generation of triangular wave using op-amp. [6]
(b) Explain the working of full wave precision rectifier with waveforms. [7]
5. (a) Draw and explain the construction of FET with its characteristics. [6]
(b) Explain how the Darlington pair improves the current gain. [6]

Or

6. (a) Draw and explain class A amplifier. [6]
(b) Explain RC coupled amplifier with neat diagram. [6]
7. (a) Explain the working of single-phase full wave rectifier with RL load. Draw input and output waveforms. [7]
(b) Compare single-phase center tap and bridge rectifiers. [6]

Or

8. (a) A half wave diode rectifier uses transformer turns ration 1 : 2 while the input voltage is $200 \sin \omega t$ and $\omega = 100 \pi$ rad/sec and the load resistance is 100Ω . [7]
Calculate :
(i) The dc output voltage
(ii) Rectification efficiency
(iii) Transformer utilization factor
(iv) Peak inverse voltage.
- (b) Draw and explain three-phase half wave rectifier with R load with adequate waveforms. [6]