

Total No of Questions: [8]

SEAT NO. :

[Total No. of Pages : 5]

S.E. 2012 (Electrical Engineering)  
NETWORK ANALYSIS  
(Semester - II)

Time: 3 Hours

Max. Marks : 50

Instructions to the candidates:

- 1) Answers Qu. 1 or 2, Qu. 3 or 4, Qu. 5 or 6, Qu 7 or 8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.
- 4) Use of Calculator is allowed.
- 5) Assume SuitableS data if necessary

Q1) a) Simplify the circuit Shown in fig (1) and. Find V

(07)

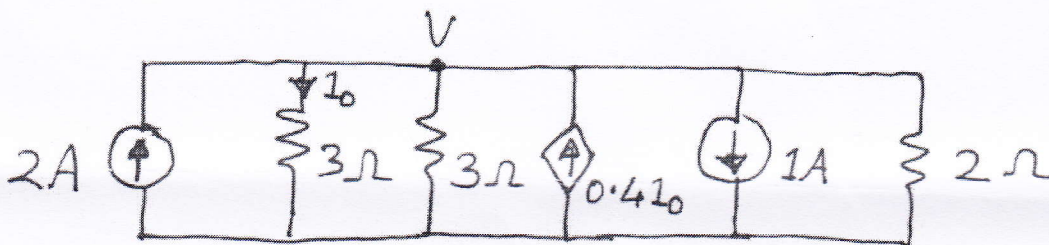


Fig (1)

b) Find current through 10 Ω resistance using mesh analysis as shown in fig (2)

(06)

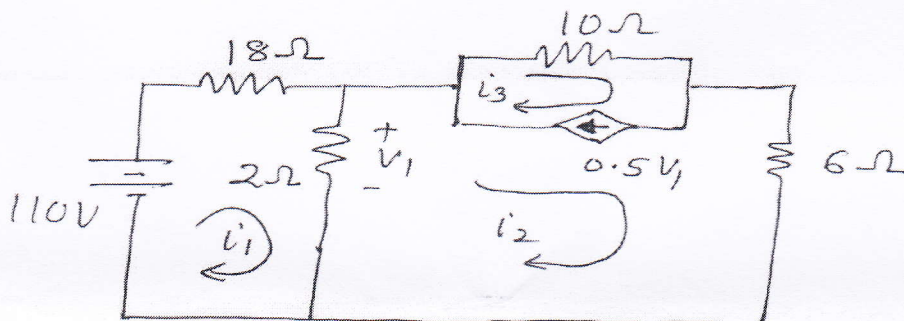


Fig (2)

OR

Q2) a) Find current through  $30\ \Omega$  resistance by using Thvenins Theorems as shown in fig (3) (07)

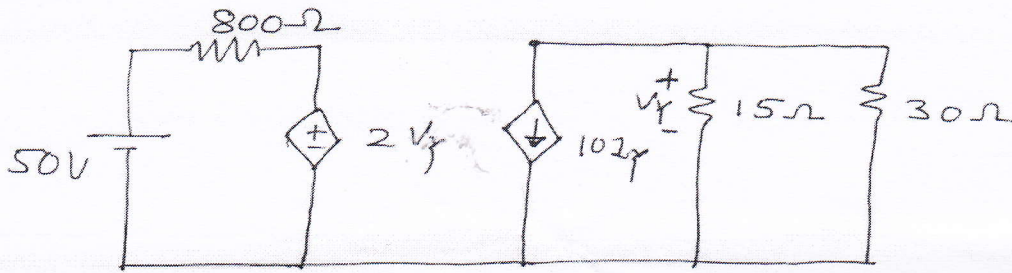


Fig. (3)

b) Find  $V_a$  and  $V_b$  by using Superposition Theorem (06)


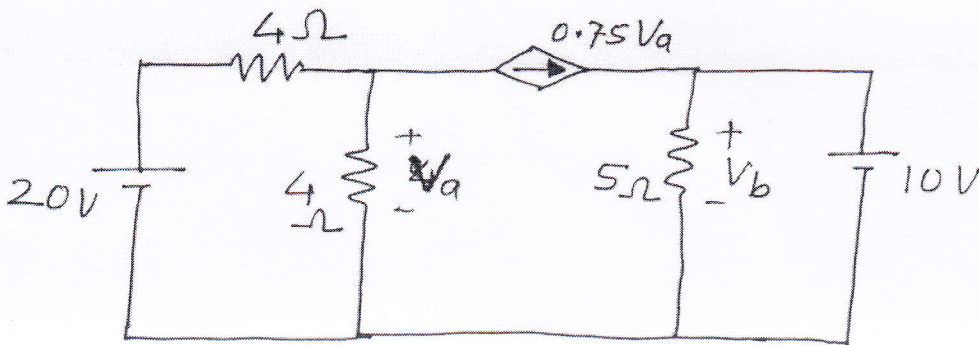


Fig. (4)

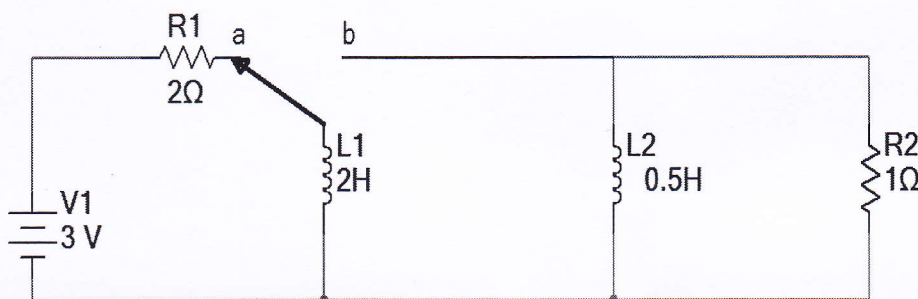Q3) a) The switch is changed from point a to b at  $t=0$ , determine voltage across 1 ohm resistance at  $t=3$  sec. (07)



Fig(5)

- b) R-L-C circuit is excited by DC voltage source. Find Current  $i(t)$  using conventional method. The switch is closed at time  $t = 0$ .

(06)

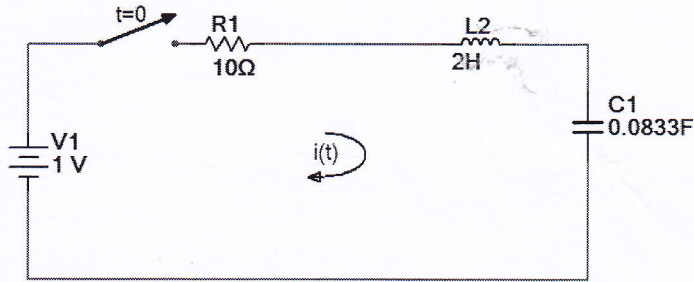


Fig (6)

OR

- Q4) a) A step d.c. current of 5 Amp. Is applied at  $t = 0$  to a parallel R-L-C circuit as shown in fig.(7). Obtain solution for voltage  $V(t)$  across circuit. Assume zero charge across capacitor.

(07)

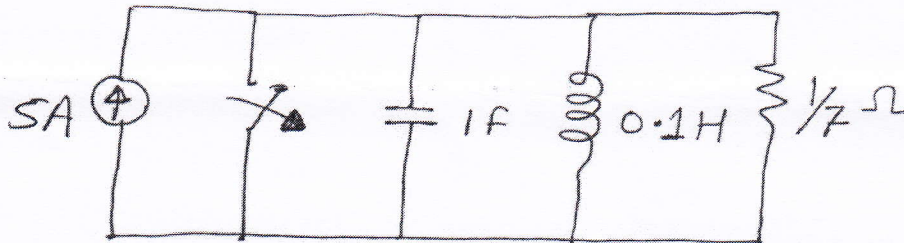


Fig (7)

- b) Obtain  $F(S)$  for the wave shown in fig. (8)

(06)


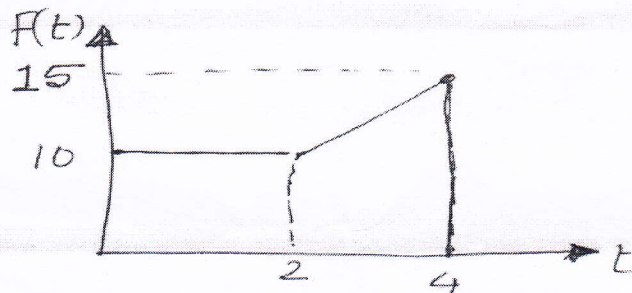
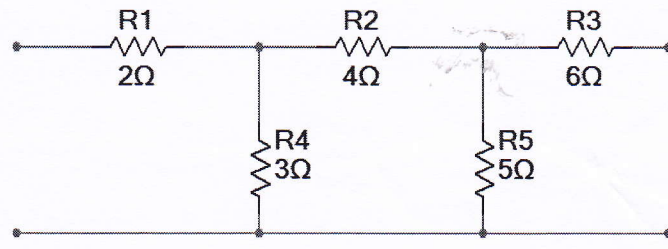
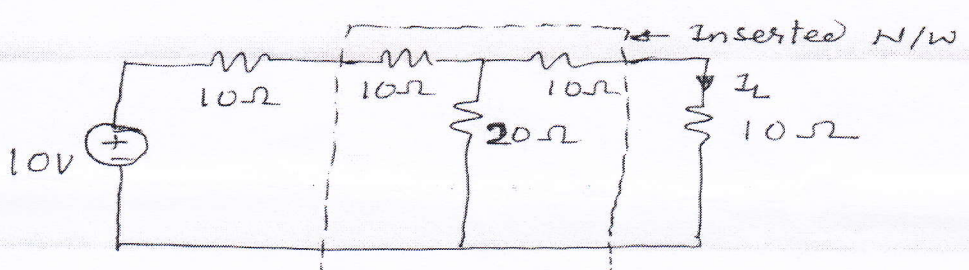


Fig. (8)

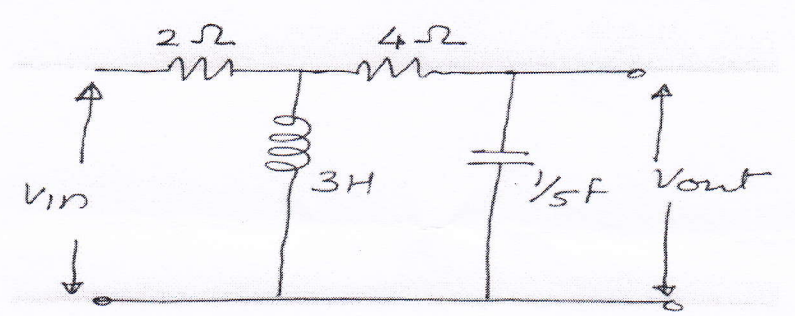

Q5)	a) A low pass filter is composed of symmetrical $\pi$ section .. Series arm is 0.02 H and each shunt arm is 2 micro farad. Find cut off frequency and designed resistance.	(06)
	b) Find Z & H parameter.of the circuit shown in fig    <p style="text-align: center;">Fig. (9)</p> <p style="text-align: center;">OR</p>	(06)
Q6)	a) In the circuit shown in fig. (10) find insertion loss in decibel in load resistance of 10 ohm    <p style="text-align: center;">Fig. (10)</p>	(06)
	b) Develop the relationship between Z parameter & Transmission line parameters	(06)
Q 7)	a) Draw poles and Zeros of transformation function for the fig. shown in fig. (11)    <p style="text-align: center;">Fig. (11)</p>	(06)

	b)	Write the notes of location of poles and corresponding transient response	
		OR	
Q)8	a)	Find the value of L at which the parallel circuit resonates at a frequency of 1000 rad./sec. in the circuit as shown in Fig 12	(06)
		Fig. 12	
	b)	Write the essential conditions of transfer function	(06)