

Total No. of Questions—8]

[Total No. of Printed Pages—4+1

| | |
|-------------|--|
| Seat No. | |
|-------------|--|

[4957]-1038

S.E. (Electrical Engineering) (Second Semester)

EXAMINATION, 2016

NETWORK ANALYSIS

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B. :-** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.
(ii) Neat diagrams must be drawn wherever necessary.
(iii) Figures to the right indicate full marks.
(iv) Use of calculator is allowed.
(v) Assume suitable data, if necessary.

SECTION I

1. (a) Find the current through 6 ohm resistance as shown in Fig. 1 by using nodal analysis method. [7]

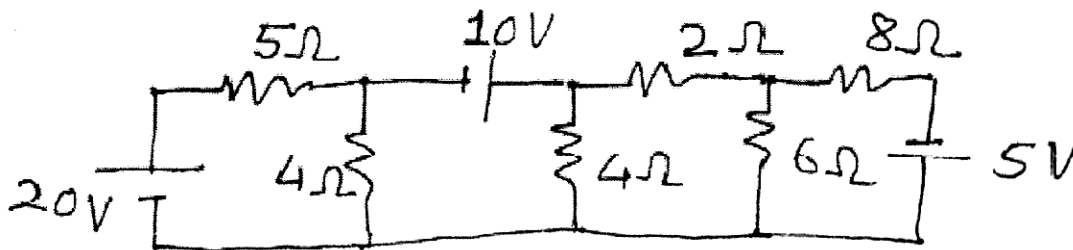


Fig. 1

P.T.O.

- (b) Find total reactance as shown in Fig. 2. [6]

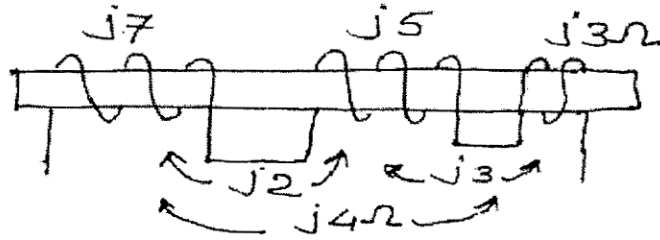


Fig. 2

Or

2. (a) Find current through 8 ohm resistance by using superposition theorem as shown in Fig. 3. [7]

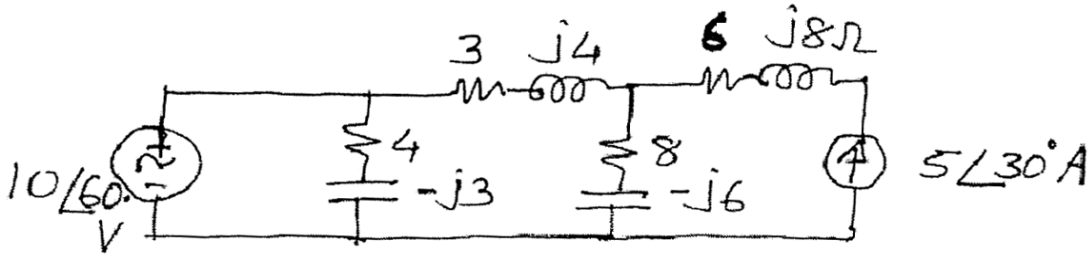


Fig. 3

- (b) Write and explain maximum power transfer theorem. Also prove the condition of maximum power transfer for DC circuit. [6]
3. (a) Using classical theory, find voltage across inductor at time $t = 2$ second, after switch is opened. [7]

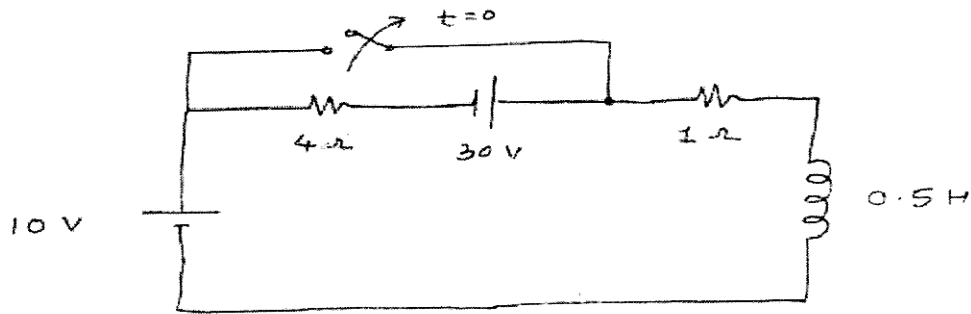


Fig. 4

- (b) Explain what you understand by critical resistance. Derive the formula. What will be general solution if resistance of network is less than and greater than critical resistance. [6]

Or

4. (a) Find the Laplace transform of the wave shown in Fig. 5. [7]

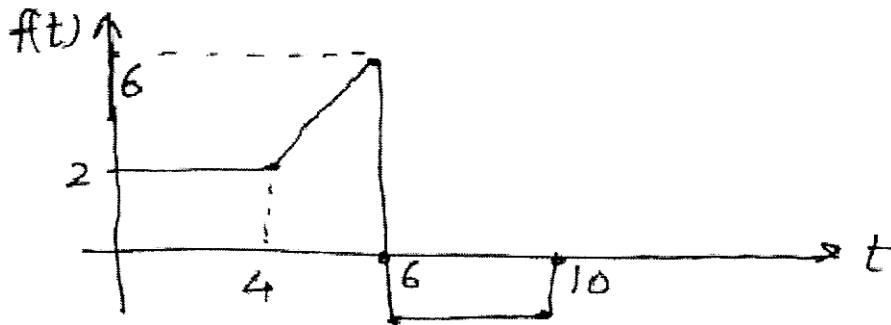


Fig. 5

- (b) Find current by using Laplace transform technique as shown in Fig. 6. [6]

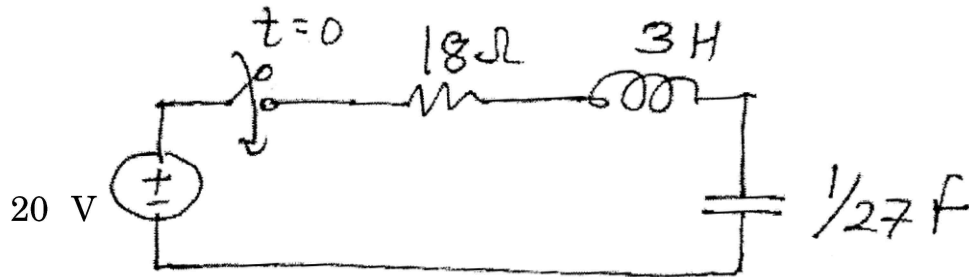


Fig. 6

5. (a) Design constant K HPF network for cut-off frequency 1 KHz, and design resistance 1000 ohm. [6]

- (b) Obtain the ABCD parameters of the circuit shown in Fig. 7. [6]

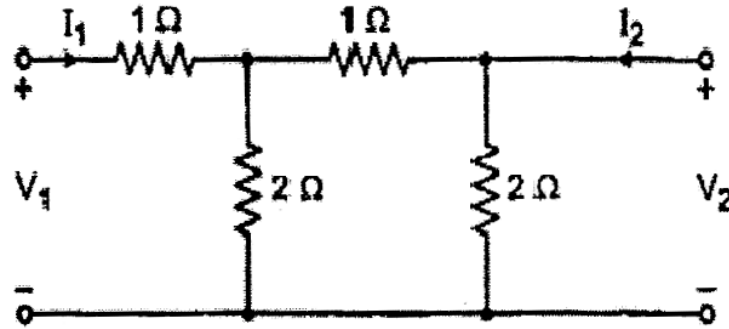


Fig. 7

Or

6. (a) In the circuit shown in Fig. 8, find Impedance parameters. [6]

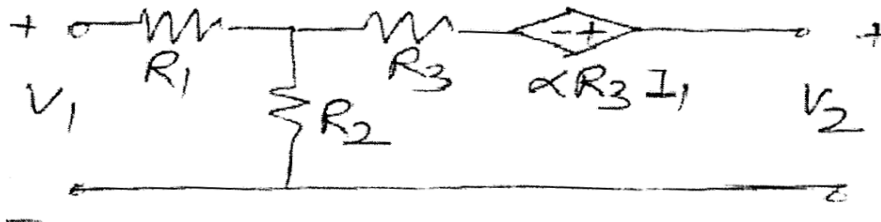


Fig. 8

- (b) Develop the relationship between Y-parameter and Hybrid parameters. [6]

7. (a) For the network shown in Fig. 9, find driving point impedance at port 1. [6]

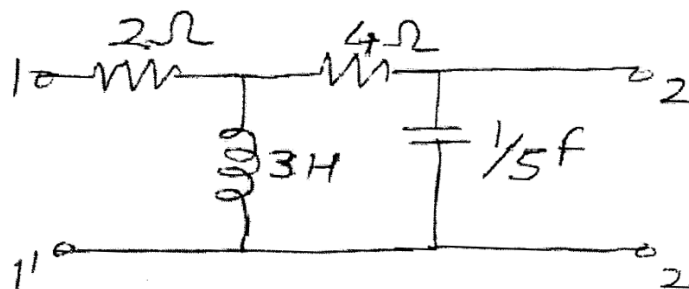


Fig. 9

- (b) A parallel resonance circuit has a coil of 150 micro henery, Quality factor = 600, resonance frequency = 1 MHz. Find :
- (i) Value of capacitance
 - (ii) Internal resistance of inductor
 - (iii) Impedance offered by circuit at resonance. [6]

Or

8. (a) Derive the impedance offered during parallel resonance condition. [6]
- (b) For the network of Fig. 10, find transfer admittance $Y_{21}(s) = I_2(s)/V_1(s)$. [6]

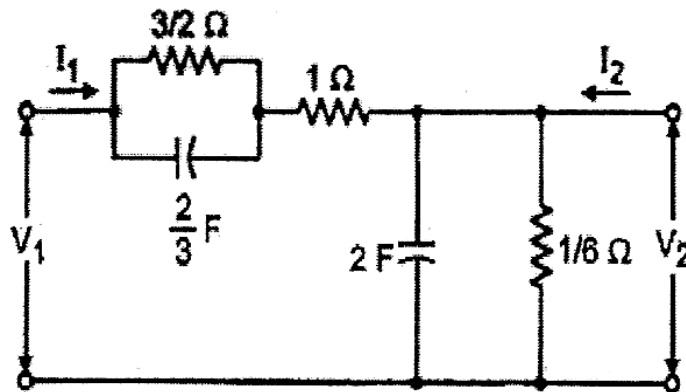


Fig. 10.