

Total No. of Questions—8]

[Total No. of Printed Pages—4+1

Seat No.	
-------------	--

[5152]-148

S.E. (Electrical Engineering) (Second Semester)

EXAMINATION, 2017

NETWORK ANALYSIS

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right side indicate full marks.

(iv) Use of calculator is allowed.

(v) Assume suitable data, if necessary.

1. (a) Reduce the given network figure 1 to a single voltage source and impedance. [7]

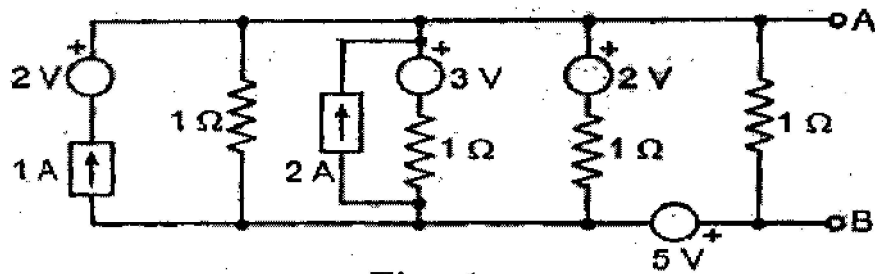


Fig. 1

P.T.O.

- (b) Find Voltage at node 1 by using Nodal Analysis technique as shown in fig. (2) [6]

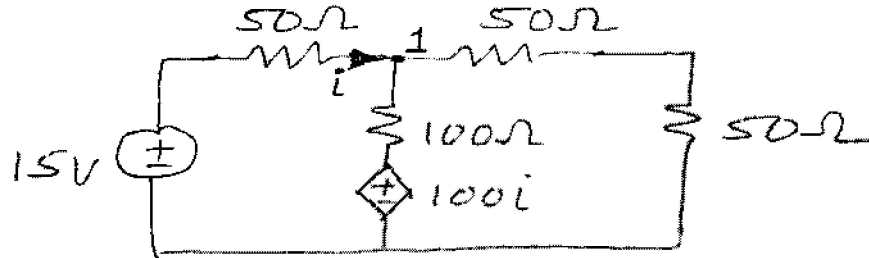


Fig. 2

Or

2. (a) Find current through $(3-j4)\ \Omega$ by using Superposition Theorems as shown in fig. (3) [7]

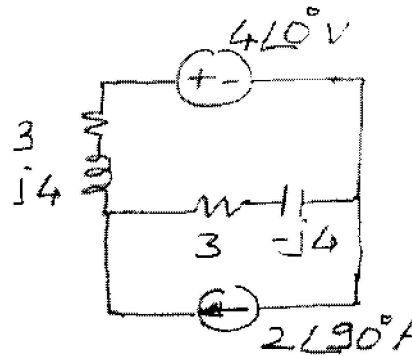


Fig. 3

- (b) Draw the dotted equivalent circuit of the coupled circuit shown and hence find voltage across capacitor by mesh analysis. [6]

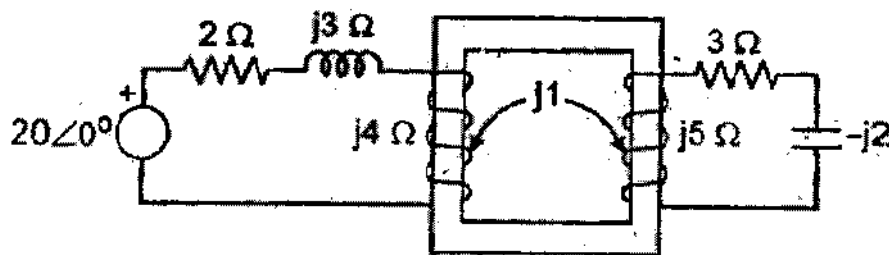


Fig. 4

3. (a) In the circuit, the switch S_1 is closed at time $t = 0$, and switch S_2 is closed at time $t = 0.1$ sec, find the transient current by using classical theory and also draw this current for two intervals. [7]

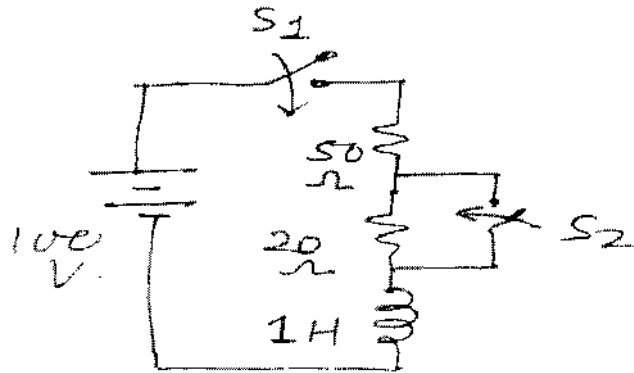


Fig. 5

- (b) R-L-C circuit is excited by DC voltage source. Find Current $i(t)$ using conventional method. The switch is closed at time $t = 0$ [6]

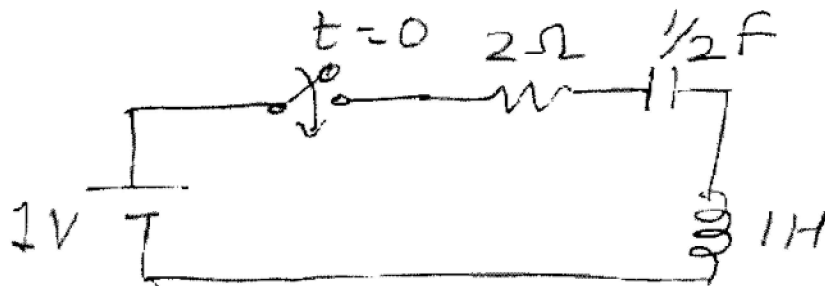


Fig. 6

Or

4. (a) After being on position 1 for long time, the switch is thrown on position 2 at time $t = 0$, find current using Laplace

Transform technique.

[7]

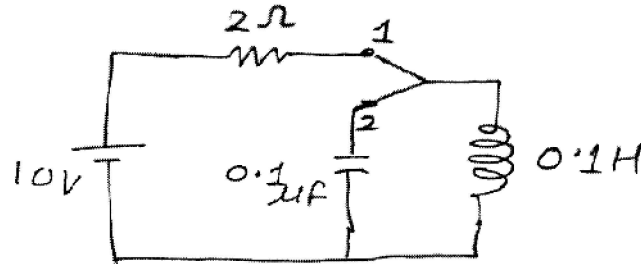


Fig. 7

- (b) Obtain $f(t)$ for the function $f(s)$, using Convolution Integral.
 $F(S) = 10/(S^2 + 7S + 12)$ [6]

5. (a) Find Z parameter for the circuit as shown in Fig. 8 [6]

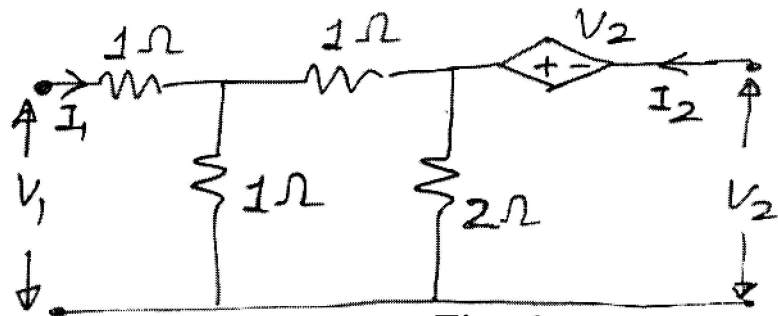


Fig. 8

- (b) In the circuit shown in Fig. 9 find insertion loss in decibel in load resistance of 10 ohm, Inserted network is shown in dotted portion. [6]

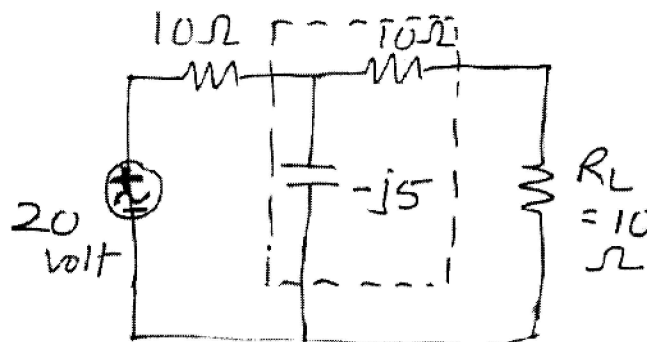


Fig. 9

Or

6. (a) Design the High pass filter and develop relation of inductance and capacitance in terms of cut-off frequency & design resistance. [6]

- (b) Obtain Z parameter of network as shown in Fig. 10. [6]

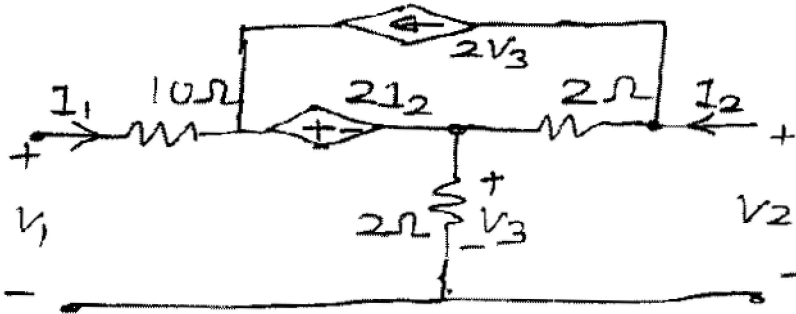


Fig. 10

7. (a) Find Transfer Function of network as shown in Fig.11. [6]

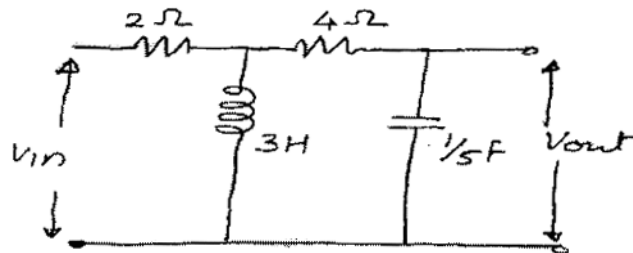


Fig. 11

- (b) A parallel resonant circuit has a coil of 120 micro henry, Quality factor is 600 and anti resonant frequency of 1 mega hertz, specify the value of capacitance, internal resistance of coil and impedance offered by circuit at resonance. [6]

Or

8. (a) For the network shown in Fig 12, find input admittance Y_{in} [6]

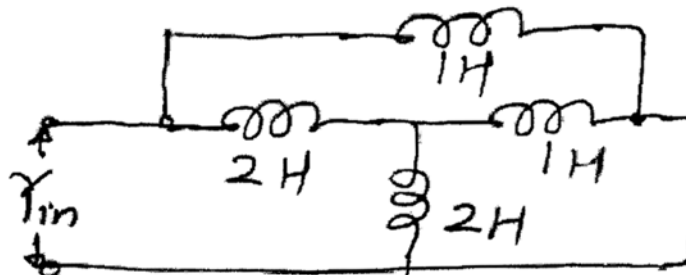


Fig. 12

- (b) Draw the time domain wave form for various types of transfer function & comment on stability of system. [6]