

Seat No.	
-------------	--

**[4857]-1038**


**S.E. (Electrical Engineering) (II Sem.) EXAMINATION, 2015  
NETWORK ANALYSIS  
(2012 PATTERN)**

**Time : Two Hours**


**Maximum Marks : 50**

- N.B. :-** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.  
 (ii) Neat diagrams must be drawn wherever necessary.  
 (iii) Figures to the right indicate full marks.  
 (iv) Use of calculator is allowed.  
 (v) Assume suitable data, if necessary.

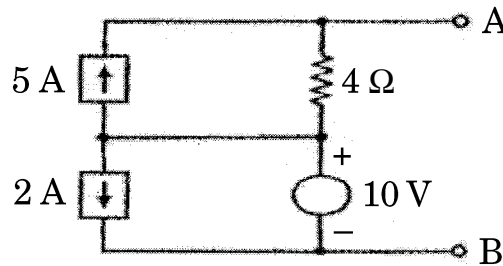1. (a) Convert the network shown in Fig. into a single voltage source in series with single resistor. [7]



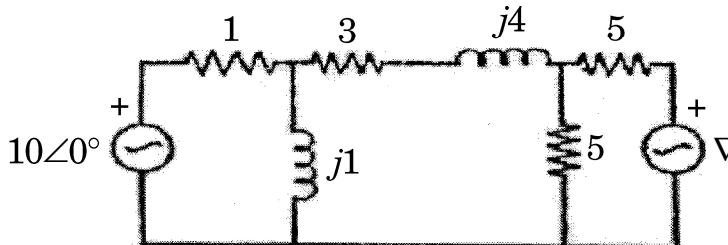
- (b) Determine  $V$  such that the current through the impedance  $(3 + j4)\Omega$  is zero. Use Thevenin's theorem. [6]




P.T.O.

Or

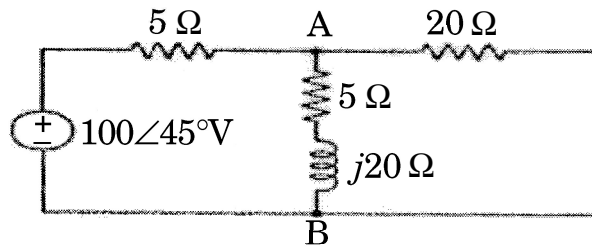
2. (a) For the network shown in figure, find the voltage  $V_{AB}$  using the nodal method. [7]



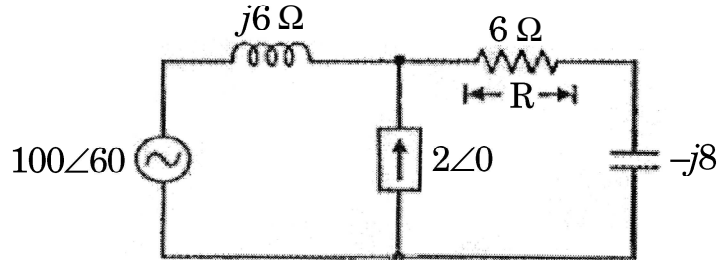
- (b) Find the current the resistor 'R' using principle of superposition. [6]



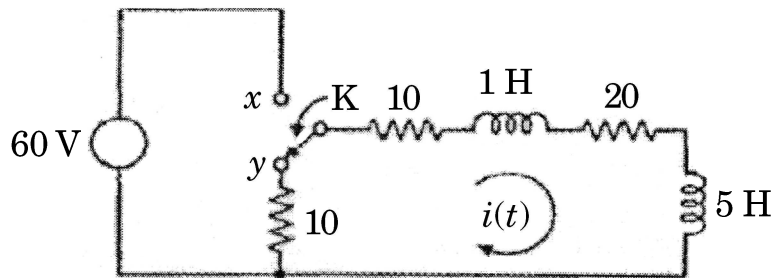3. (a) Find particular solution for  $i(t)$  when switch K is moved from  $x$  to  $y$  at time  $t = 0$ . Steady state current having previously obtained in Circuit use conventional method. [7]




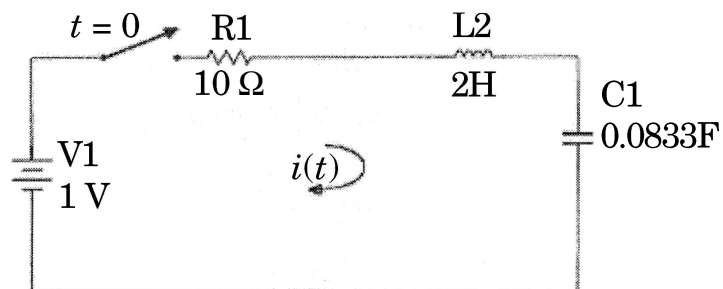- (b) R-L-C circuit is excited by DC voltage source. Find Current  $i(t)$  using conventional method. The switch is closed at time  $t = 0$ . [6]




Or

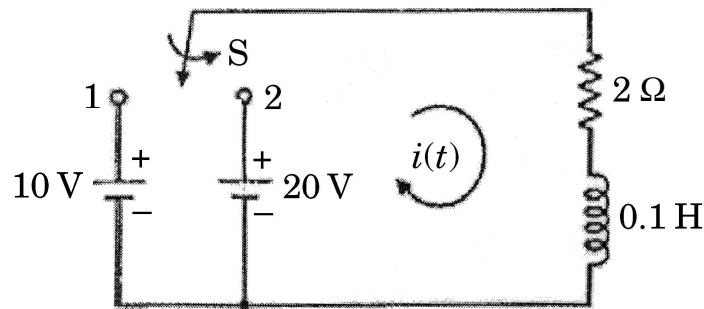4. (a) For the circuit shown in Fig. below, determine the current  $i(t)$ , when the switch is moved, from position 1 to position 2 at  $t = 0$ . The switch has been at position 1 for a long time to get the steady state values. Use Laplace transform method. [7]




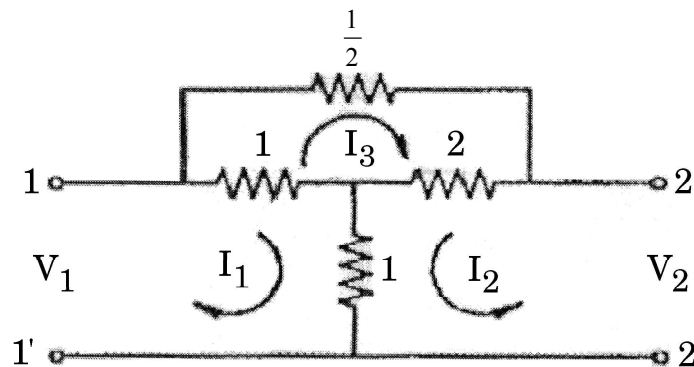- (b) Obtain the inverse Laplace transform of  $F(s) = 1/s(s + 2)$  by using convolution integral. [6]
5. (a) Design constant K HPF network for cutoff frequency 1 kHz and design resistance 1000 ohm. [6]
- (b) For the network shown in Fig. below, find Z parameters. [6]




Or

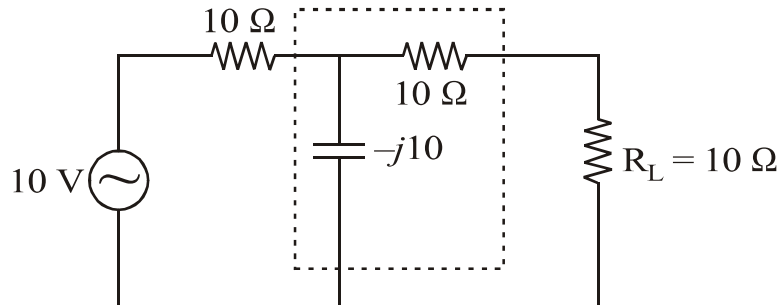6. (a) In the circuit shown in Fig. below, find insertion loss in decibel in load resistance of 10 ohm. [6]



- (b) Develop the relationship between Transmission and Hybrid Parameters. [6]

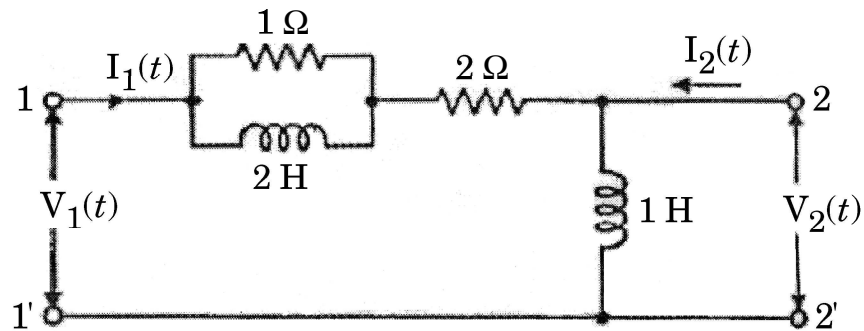
7. (a) The network in figure, is terminated at port 2 by a resistance of 1 ohm. Find the transform admittance  $Y_{12} = I_2(s)/V_1(s)$  for the network. [6]



- (b) Define the following terms : [6]
- (i) Transfer functions
  - (ii) Voltage transfer ratio
  - (iii) Current transfer-ratio
  - (iv) Transfer admittance
  - (v) Transfer impedance.

Or

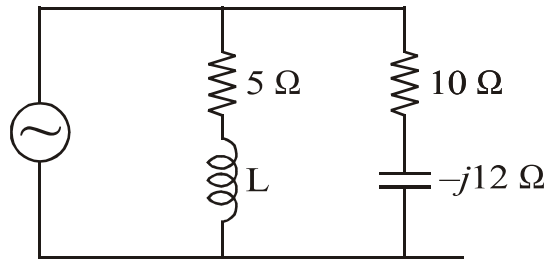8. (a) Find the value of  $L$  at which the parallel circuit resonates at a frequency of  $1000 \text{ rad./sec.}$  in the circuit as shown in Fig. [6]



- (b) Write the essential conditions of transfer function. [6]