

Total No. of Questions—8]

[Total No. of Printed Pages—6

Seat No.	
----------	--

[5057]-238

S.E. (Electrical Engineering) (Second Semester)

EXAMINATION, 2016

NETWORK ANALYSIS

(2012 PATTERN)

Time : Three Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6 and Q. 7 or Q. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right side indicate full marks.

(iv) Use of calculator is allowed.

(v) Assume suitable data, if necessary.

1. (a) Simplify the circuit shown in Fig. 1 and find V. [7]

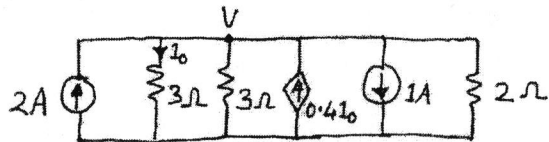


Fig. 1

P.T.O.

(b) Find Voltage at node 1 by using Nodal Analysis technique as shown in Fig. 2. [6]

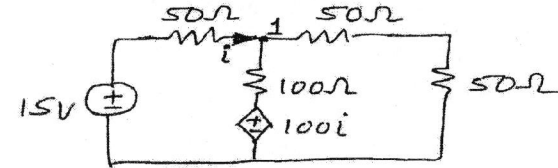


Fig. 2

Or

2. (a) Find  $V_a$  and  $V_b$  by using Superposition Theorem. [7]

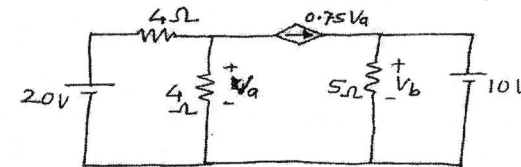


Fig. 3

(b) Draw the dotted equivalent circuit of the coupled circuit shown and hence find voltage across capacitor by mesh analysis. [6]

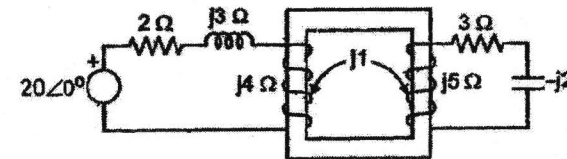


Fig. 4

[5057]-238

2

3. (a) In the circuit, the switch S1 is closed at time  $t = 0$ , and switch S2 is closed at time  $t = 0.1$  sec, find the transient current by using classical theory and also draw this current for two intervals. [7]

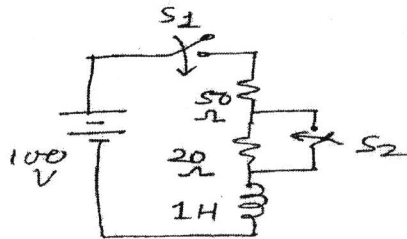


Fig. 5

- (b) R-L-C circuit is excited by DC voltage source. Find current  $i(t)$  using conventional method. The switch is closed at time  $t = 0$ . [6]

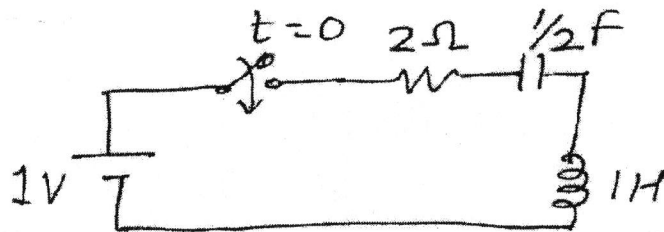


Fig. 6

Or

4. (a) After being on position 1 for long time, the switch is thrown on position 2 at time  $t = 0$ , find current using Laplace Transform technique. [7]

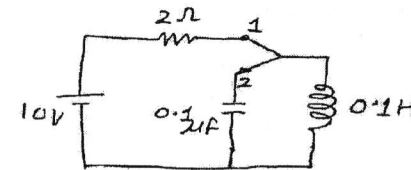


Fig. 7

- (b) Obtain  $f(t)$  for the function  $f(s)$ , using Convolution Integral : [6]

$$F(S) = 1/(S^2 + 20S + 75).$$

5. (a) Find Z parameter for the circuit as shown in Fig. 8. [6]

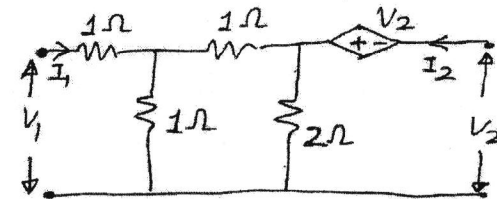


Fig. 8

- (b) In the circuit shown in Fig. 9 find insertion loss in decibel in load resistance of 10 ohm, inserted network is shown in dotted portion. [6]

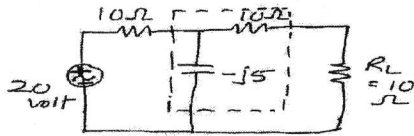


Fig. 9

Or

6. (a) Design the low pass filter and develop relation of inductance and capacitance in terms of cut-off frequency and design resistance. [6]
- (b) For the network shown in Fig. 10. Find Z parameters. [6]

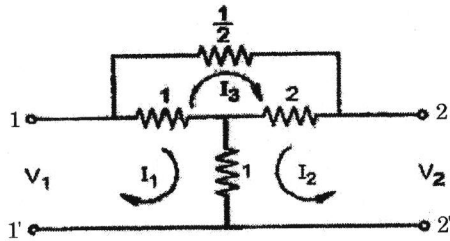


Fig. 10

7. (a) Find Voltage Transfer function. [6]

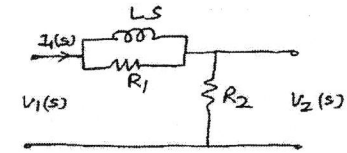


Fig. 11

- (b) A parallel resonant circuit has a coil of 150 micro henry, Quality factor is 800 and anti-resonant frequency of 1.2 mega hertz. Specify the value of capacitance, internal resistance of coil and impedance offered by circuit at resonance. [6]

Or

8. (a) For the network shown in Fig. 12, find input admittance  $Y_{in}$ . [6]

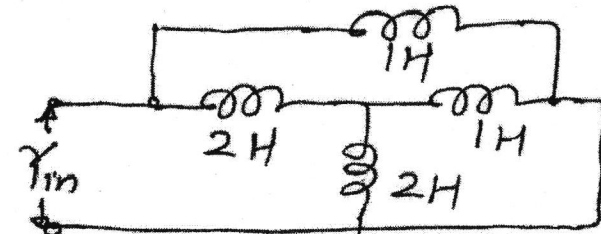


Fig. 12

- (b) Draw the time domain wave form for various types of transfer function and comment on stability of system. [6]