

Total No. of Questions—8]

[Total No. of Printed Pages—6

Seat No.	
-------------	--

[5252]-148

**S.E. (Electrical Engineering) (Second Semester)**

**EXAMINATION, 2017**

**NETWORK ANALYSIS**

**(2012 PATTERN)**

**Time : Two Hours**

**Maximum Marks : 50**

**N.B. :-** (i) Answers Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,  
Q. No. 5 or Q. No. 6. Q. No. 7 or Q. No. 8.


(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right side indicate full marks.

(iv) Use of calculator is allowed.

(v) Assume suitable data if necessary.

1. (a) Reduce the given network figure to a single voltage source and impedance. [6]

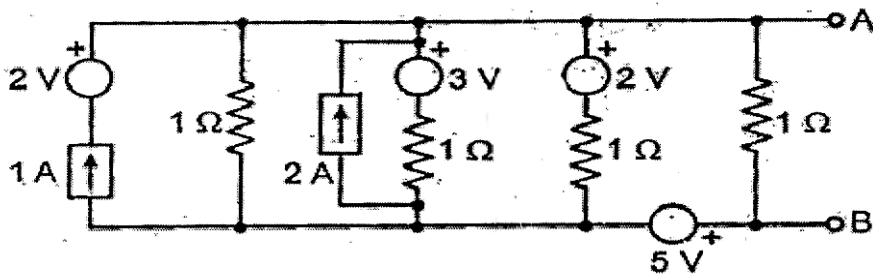

**Fig. 1**

P.T.O.

- (b) Obtain Norton's equivalent network between terminals A and B as shown in fig.2. [7]

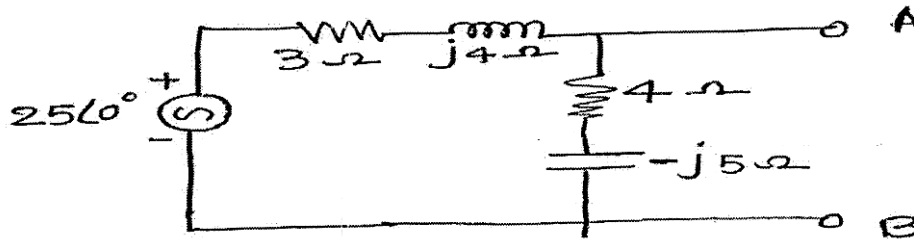


Fig. 2

Or

2. (a) Find current through  $(3 - j4) \Omega$  by using Thvenin's Theorems as shown in fig (3). [7]

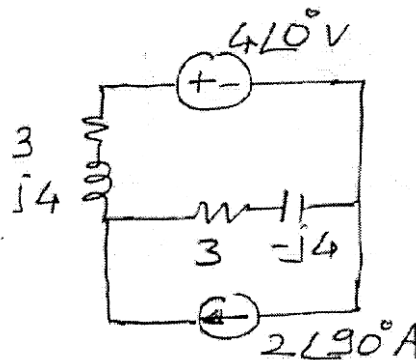


Fig. 3

- (b) Find current through 5 ohm resistance by using Kirchhoff's voltage law. [6]


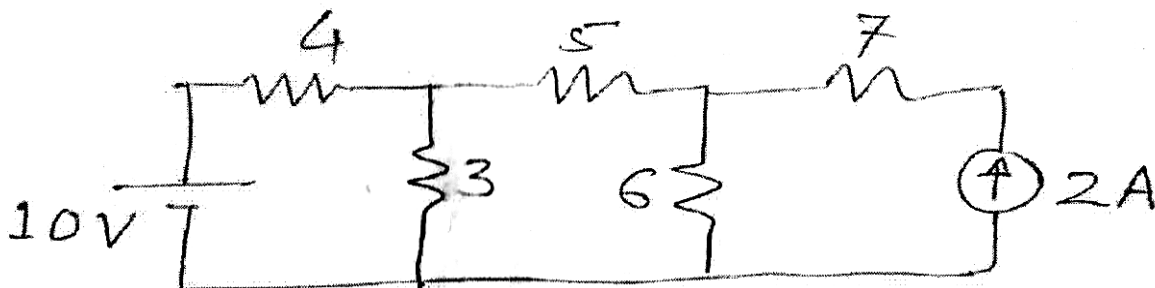



Fig. 4

3. (a) Find voltage  $V$  for  $t = 0.1$  sec. after closing the switch at  $t = 0$ .

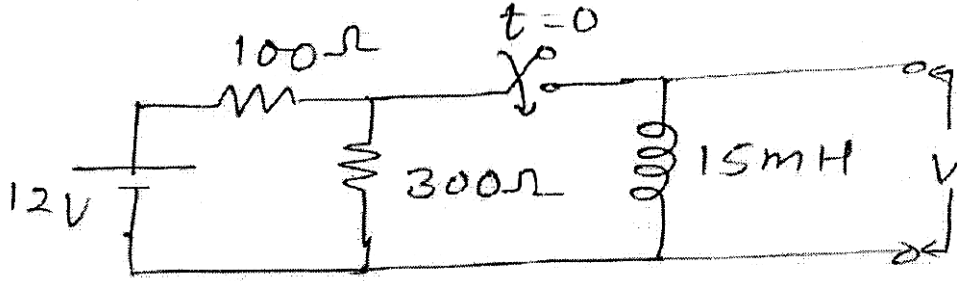


**Fig. 5**

- (b) Write short note on initial and final condition, justify your answer. [6]
- Or
4. (a) After being on position 1 for long time, the switch is thrown on position 2 at time  $t = 0$ , find current using Laplace Transform technique. [7]

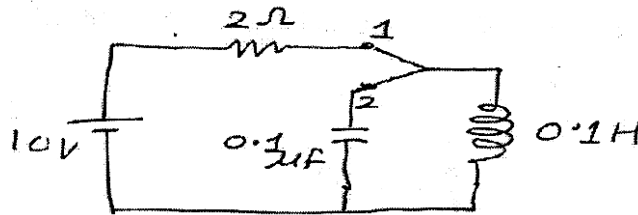

**Fig. 6**

- (b) The switch is closed at time  $t = 0$ , obtain the particular solution for current  $i(t)$  using Laplace Transform technique. Assume initial condition is zero. [6]

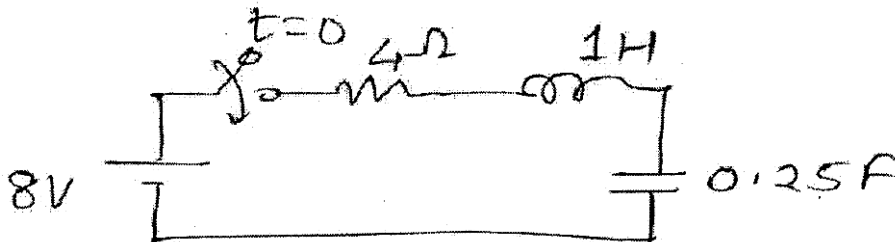

**Fig. 7**

5. (a) Find Z parameter for the circuit as shown in fig. 8. [6]

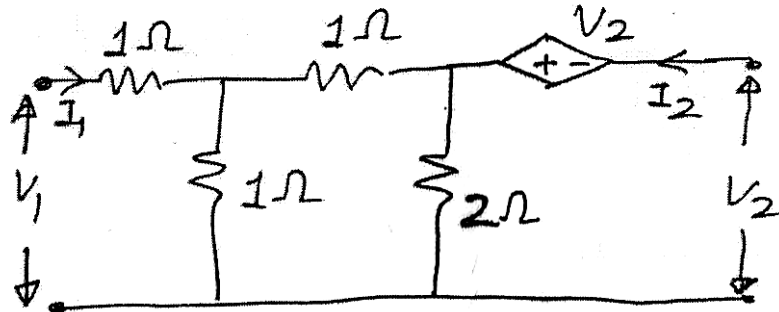


Fig. 8

- (b) In the circuit shown in fig.(9) find insertion loss in decibel in load resistance of 10 ohm, Inserted network is shown in dotted portion. [6]

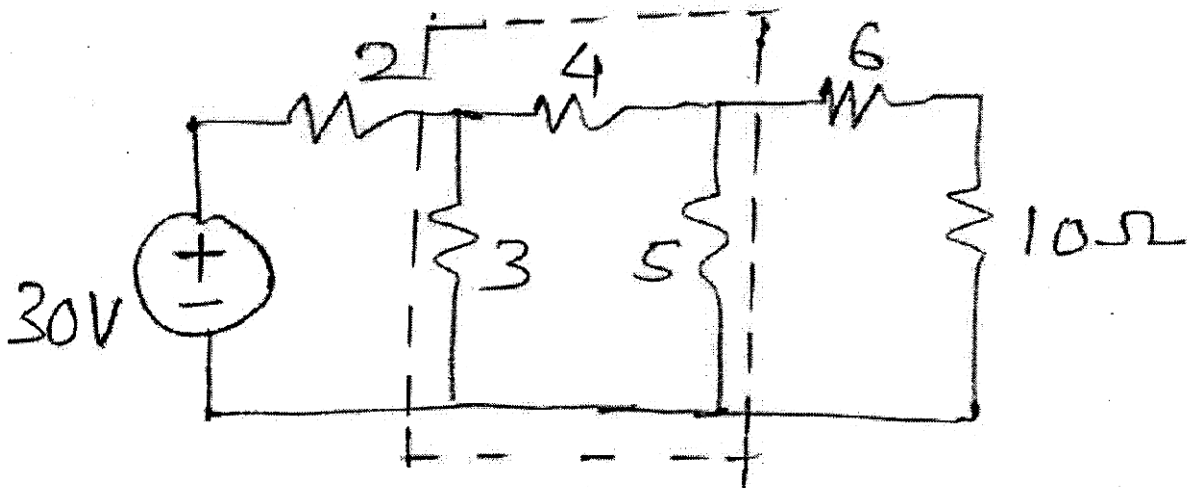


Fig. 9

6. (a) If a constant k high-pass filter has cut-off frequency of 13 kHz and nominal impedance of  $R_0 = 600 \text{ ohm}$ , design the T and  $\pi$  sections of this filter. [6]
- (b) Obtain Z parameter of network as shown in fig (10). [6]

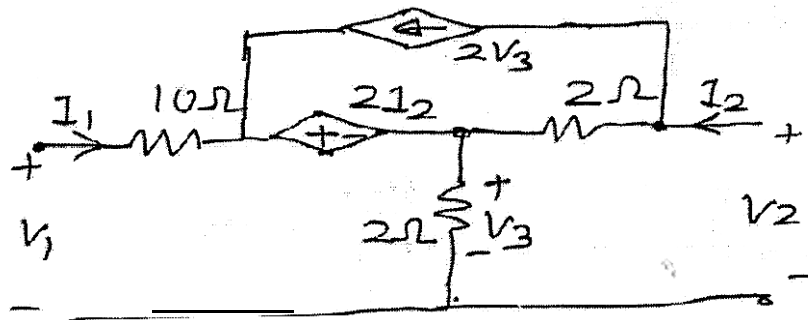


Fig. 10

7. (a) Find Transfer Function of network as shown in fig. (11). [6]


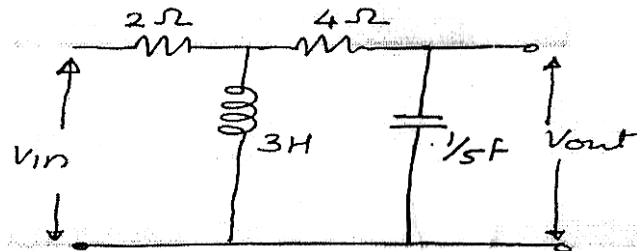


Fig. 11

- (b) Draw the time domain wave form for various types of transfer function and comment on stability of system. [6]

8. (a) Find poles and zero of the impedance of the following network and plot them on the  $s$  – plane in fig. 12. [6]

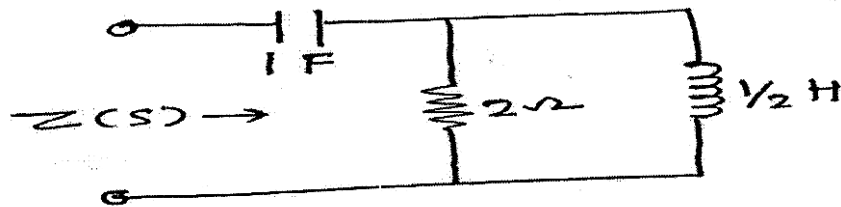

**Fig. 12**

- (b) Explain parallel resonance, condition drive the formula for anti-resonant frequency. [6]