

Seat No.	
-------------	--

[5252]-132

S.E. (E&TC/Electronics) (First Semester) EXAMINATION, 2017
ELECTRONIC DEVICES AND CIRCUITS
(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B. :**— (i) Attempt Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6 and Q. No. 7 or Q. No. 8.
(ii) Neat diagrams must be drawn wherever necessary.
(iii) Figures to the right indicate full marks.
(iv) Use of scientific calculator is allowed.
(v) Assume suitable data, if necessary.

1. (a) What is operating point ? Explain its significance with d.c. load line. Also, state why voltage divider bias with emitter resistor is preferred over other biasing methods. [6]
(b) Calculate A_v , R_i , R_o for the CE amplifier as shown in Fig. 1. Given : $h_{re} = h_{oe} = 0$, $h_{ie} = 1 \text{ k}\Omega$, $h_{fe} = 350$. [7]

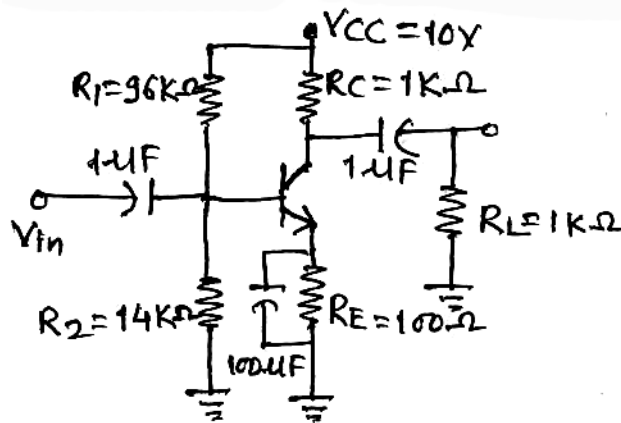


Fig. 1

P.T.O.

Or

2. (a) Define various stability factors and explain its significance with necessary equations. [6]
(b) Explain the significance of hybrid parameters in BJT. [3]
(c) Compare CE, CB, CC on the basis of R_i , R_o and their applications. [4]
3. (a) For a cascaded two stage amplifier using identical transistors, find lower and higher cutoff frequencies and bandwidth. The h -parameters for the transistors are $h_{ie} = 1.1 \text{ k}\Omega$, $h_{fe} = 250$, $h_{re} = h_{oe} = 0$. The lower cutoff frequency of single stage is 100 Hz and higher cutoff frequency in 15 KHz. [6]
(b) Draw all the four topological block diagram for -ve feedback amplifiers. State application of each of the amplifier. [6]

Or

4. (a) The parameters of the transistors in the ckt shown in Fig. 2 are $h_{fe} = 50$, $h_{ie} = 1.1 \text{ k}\Omega$, $h_{re} = h_{oe} = 0$. Find : [6]
(i) Value of C_b for 3-dB frequency response of 20 Hz
(ii) Value of C_b necessary to ensure less than 10% till for 100 Hz square wave 1/p.

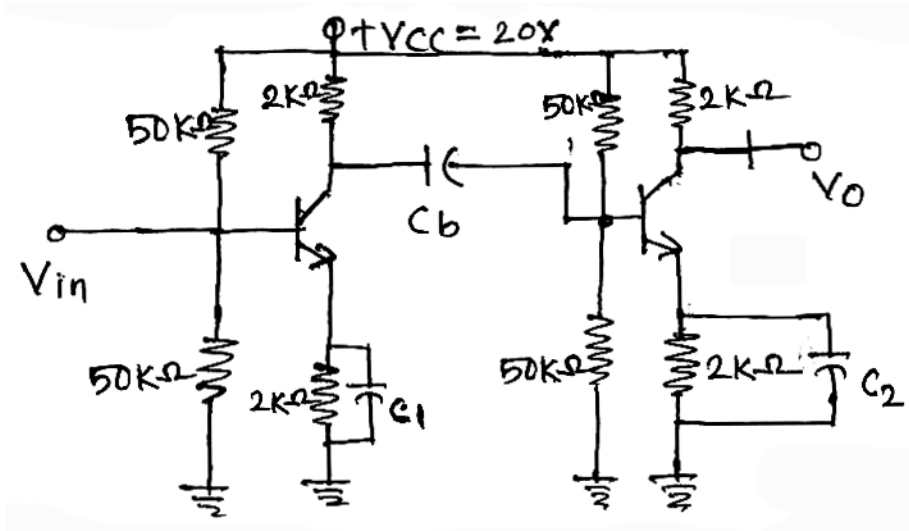


Fig. 2

(b) State Barkhausen criterion. Find frequency of oscillation for LC oscillator with $L_1 = 1 \mu\text{H}$, $L_2 = 3 \mu\text{H}$, $C = 0.01 \mu\text{F}$. Also identify the name of oscillator and state the application of the oscillator. [6]

5. (a) Write a short note on power BJTs. [6]

(b) For class-B amplifier providing 20 V peak signal to 16Ω load (speaker) and power supply of 30 V. Determine the 1/P power, O/P power and efficiency. [7]

Or

6. (a) A sinusoidal signal $V_s = 1.95 \sin 400 t$ is applied to a power amplifier. The resulting current is

$$i_0 = 12 \sin 400 t + 1.2 \sin 800 t + 0.9 \sin 1200 t + 0.4 \sin 1600 t.$$

Calculate :

(i) total harmonic distortion

(ii) %age increase in power due to distortion. [7]

(b) Draw a single power supply class AB complimentary push-pull amplifier and explain how cross-over distortion is eliminated in this amplifier with wave forms. [6]

7. (a) Plot transfer and drain characteristics of n-channel E-MOSFET with necessary static and dynamic parameters. State equation for saturated current. [7]

(b) What is constant current source biasing ? Explain with circuit diagram in detail. [6]

Or

8. (a) Explain the effect of substrate potential in MOS based on integrated circuits. Also, explain the effect of channel length modulation. [6]
- (b) Find I_D , V_{DS} , V_{GS} for the circuit shown in Fig. 3. Given $V_{Th} = 0.8 \text{ V}$, $K = 1 \text{ mA/V}^2$, $\lambda = 0$. [7]

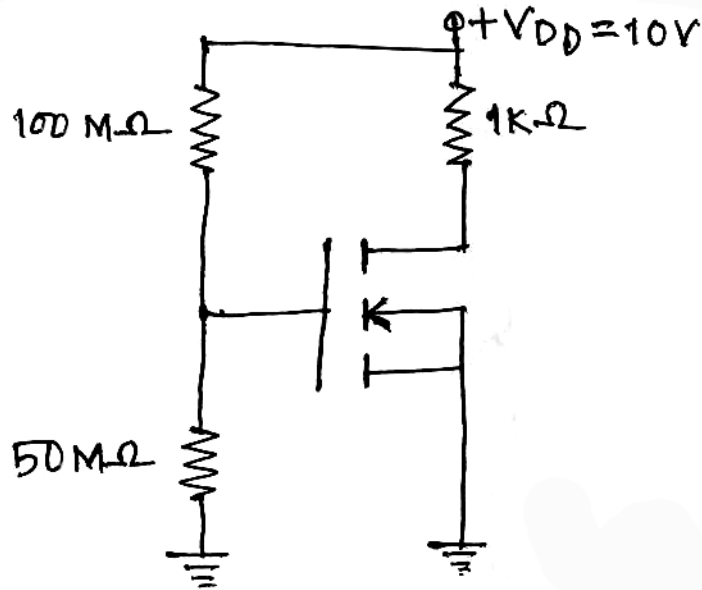


Fig. 3