

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
---------------------	--

[5668]-136

S.E. (E&TC/Electronics) (I Sem.) EXAMINATION, 2019

ELECTRONIC DEVICES AND CIRCUITS

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.

(ii) Neat diagram must be drawn wherever necessary.

(iii) Use of logarithm tables, slide rule, Mollier charts, electronic pocket calculator and steam table is allowed.

(iv) Assume suitable data, if necessary.

1. (A) State and explain the stability factors. [6]

(B) Draw the circuit diagram of single stage CE amplifier and explain with suitable waveforms. [7]

Or

2. (A) What is thermal runaway ? Explain the thermal stability conditions. [6]

(B) Consider single stage CE amplifier with $R_1 = 50 \text{ K}\Omega$, $R_2 = 2 \text{ K}\Omega$, $R_C = 2 \text{ K}\Omega$, $R_L = 2 \text{ K}\Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \text{ uA/V}$ and $h_{ie} = 1.1 \text{ K}\Omega$. Calculate : A_v , R_i , R_o . [7]

P.T.O.

3. (A) Explain the concept of frequency response of CE amplifier with justification. [6]
- (B) Explain the general characteristics of negative feedback amplifier. [6]

Or

4. (A) Draw and explain the hybrid π Model of common emitter (CE) amplifier Model. [6]
- (B) State the Barkhausen criteria. Draw the colpitts oscillator and explain it. [6]

5. (A) Compare the different types of large signal amplifiers. [6]
- (B) What is crossover distortion ? Explain the method to overcome the crossover distortion. [7]


Or

6. (A) Draw and explain the vertically oriented structure of power BJT. [6]
- (B) Draw and explain the Class B push pull power amplifier. State the merits and demerits of it. [7]

7. (A) Explain the following non-ideal characteristics of MOSFET : [6]
1. Finite output resistance
 2. Sub threshold conduction
 3. Body effect.
- (B) Write a short note on Bi-CMOS technology. [6]

Or

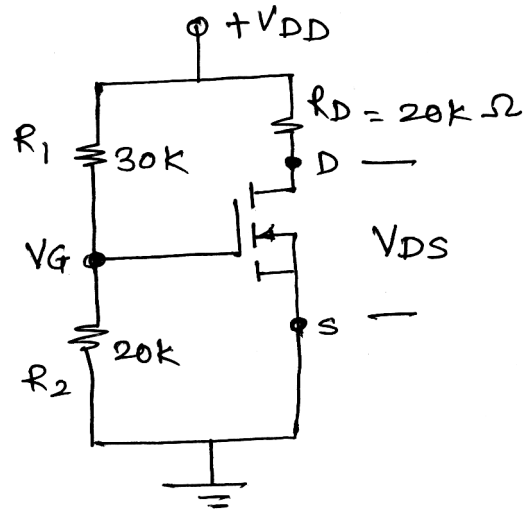8. (A) Draw the common source E-MOSFET amplifier & explain its modes of operation in detail with equation. [6]
- (B) For the circuit shown in fig. 1, calculate I_{DQ} , V_{DSQ} . [6]



Assume :

$$V_{TN} = 1 \text{ V}$$

$$K_n = 0.1 \text{ mA/V}^2.$$