

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[4757]-1050

S.E. (Elex/E & TC) (First Semester) EXAMINATION, 2015

DIGITAL ELECTRONICS

(2012 Pattern)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Figures to the right indicate full marks.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Assume suitable data, if necessary.

1. (a) Draw and explain the working of two input TTL NAND gates (with totem pole). [6]

(b) Implement the following function using single 8 : 1 MUX. [6]

$$F(A, B, C, D) = \sum m (1, 4, 6, 8, 10, 11, 13, 14)$$

Or

2. (a) Design and implement full adder using suitable decoder. [6]

(b) Draw and explain the working of 2 i/p CMOS NOR gate. [6]

P.T.O.

3. (a) Design mod 6 ripple up counter using T flip-flops. [6]
(b) Convert D to T and vice versa. [6]

Or

4. (a) Explain moore circuit with example. Also compare moore and mealy circuit. [6]
(b) Design a sequence detector to detect sequence 1101 using D FF and mealy machine. [6]
5. (a) Compare between PROM and PAL. [5]
(b) A combinational circuit is defined by a function $F_1 = \Sigma m(1, 3, 5)$
 $F_2 = \Sigma m(5, 6, 7)$.

Implement the circuit with PLA having 3 inputs, 3 product terms and two outputs. [8]

Or

6. (a) Explain in detail the architecture of CPLD. [6]
(b) What is meant by EPROM ? State its advantages and disadvantages. [7]
7. (a) Explain the following statements with examples : [6]
(i) Process
(ii) Case
(iii) If else

- (b) Write a VHDL code for 8 : 1 multiplexer using behavioural modeling. [7]

Or

8. (a) Explain in detail signal and variable with example in VHDL. [6]
- (b) Write a VHDL code for 4-bit ALU using case statement. [7]