

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5352]-136

S.E. (E&TC/Elect.) (II Sem.) EXAMINATION, 2018
INTEGRATED CIRCUITS
(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B. :-** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.
(ii) Neat diagrams must be drawn wherever necessary.
(iii) Figures to the right indicate full marks.
(iv) Use of electronic pocket calculator is allowed.
(v) Assume suitable data, if necessary.

Q.1 (a) Draw the block diagram of op-amp and explain the function of each block in detail. [04]

(b) Define the following op-amp parameters. [04]

- 1) Slew rate
- 2) CMRR
- 3) Input offset voltage
- 4) PSRR

(c) State and compare different op-amp technologies. [04]

OR

Q.2 (a) What is the need of frequency compensation? Explain any one method of external frequency compensation. [06]

(b) The dual input balanced output difference amplifier has following specifications. [06]

$R_C = 2.5k\Omega$, $R_E = 4.8k\Omega$, $R_{b1} = R_{b2} = R_b = 50\Omega$, $+V_{CC} = +10V$, $-V_{EE} = -10V$, $\beta = 100$,
 $V_{BE} = 0.8V$. Assume $h_{ie} = 1.1k\Omega$. Calculate:


- 1) Q-point values
- 2) Voltage gain
- 3) Input & Output Resistance

P.T.O.

- Q. 3 (a)** Why ideal integrator is required to be modified? Draw the practical integrator and explain its operation with frequency response. **[06]**
- (b)** Draw and explain precision half wave rectifier circuit using op-amp. **[04]**
- (c)** List out the characteristics of a typical/good instrumentation amplifier. **[02]**

OR

 - Q. 4 (a)** For the Inverting Schmitt trigger shown below, Calculate UTP, LTP & hysteresis width. Draw input & output waveforms. Also comment on Hysteresis loop. **[06]**



- (b)** Draw a neat circuit diagram of two inputs inverting summing amplifier using op-amp & obtain expression for output voltage. **[06]**
- Q. 5 (a)** Draw the circuit diagram and explain working of voltage mode R-2R ladder DAC. **[05]**
- (b)** Explain grounded load V to I converter with necessary derivation. **[04]**
- (c)** Explain current to voltage converter using Op-amp. **[04]**
- OR**
- Q. 6 (a)** Write a note on 2 bit Flash type analog to digital converter (ADC). **[06]**
- (b)** A 5 bit R-2R ladder network with reference voltage of 10V. Find **[07]**
- 1) Analog output due to LSB change.
 - 2) Full scale output voltage
 - 3) Analog output for digital input 11001
- Q. 7 (a)** Explain the operation of PLL using a neat block diagram. Define the terms Centre frequency and capture time related to PLL. **[06]**

(b) Explain low drop-out regulator. [04]

(c) Explain frequency multiplier using PLL. [03]

OR

Q. 8 (a) Calculate output frequency f_o , lock range and capture range of PLL if the timing parameters are $C_T=0.1\mu\text{f}$, $R_T=1\text{k}\Omega$. The filter capacitor is $10\mu\text{f}$. [06]

(b) Draw a neat diagram and explain three terminal adjustable voltage regulator with expression for output voltage. [07]