

Total No. of Questions—8]

[Total No. of Printed Pages—4

Seat No.	
---------------------	--

[4657]-546

S.E. (E&TC/Electronics) (Second Semester) EXAMINATION, 2014

INTEGRATED CIRCUITS

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6 and
Q. 7 or Q. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Use of calculator is allowed.

(v) Assume suitable data, if necessary.

1. (a) Define the following characteristics of practical op-amp : [6]

(i) Input offset voltage

(ii) CMMR

(iii) PSSR

(iv) Slew rate.

P.T.O.

- (b) What is slew rate ? What are its causes ? Derive its expression for maximum frequency of operation for a desire output swing in terms of slew rate. [6]

Or

2. (a) Justify, how constant current source is used in place of R_E to improve the CMRR for a differential amplifier. [6]
- (b) What is need for frequency compensation ? State and explain Pole—Zero compensation method of frequency compensation. [6]
3. (a) Why basic Integrator is needed to be modified ? Draw the circuit diagram of Practical Integrator along with frequency response and explain its operation. [6]
- (b) List important characteristics of Comparator ? What are the advantages of Schmitt trigger over Comparator ? [6]

Or

4. (a) Draw circuit diagram of Three op-amp Instrumentation Amplifier and write its output equation. [6]
- (b) Design a Schmitt trigger for $U_{TP} = 3V$ and $L_{TP} = -2V$ with general purpose op-amp 741. Assume $V_{CC} = +/-12V$. Draw detailed diagram with designed values. [6]

5. (a) Draw a neat schematic of Voltage Controlled Oscillator (VCO) using Op-amp. Derive the expression for output frequency. [6]
- (b) With the help of a neat block diagram, explain operation of Phase Locked Loop (PLL). Define the term “Lock Range” and “Capture Range”. [7]

Or

6. (a) Explain Voltage to Current Converter with grounded load using Op-amp and give its applications. [6]
- (b) Define “Lock Range”, “Capture Range” and “Pull-in time” and explain the transfer characteristics of Phase Locked Loop (PLL). [7]
7. (a) Draw the circuit diagram of Voltage mode R—2R ladder Digital to Analog converter (DAC) and explain its working. [7]
- (b) Calculate output frequency ' f_o ', Lock range ' Δf_L ', Capture range ' Δf_C ' of a PLL, If $R_T = 1 \text{ k}\Omega$, $C_T = 0.1 \text{ }\mu\text{f}$ and filter capacitor $C = 10 \text{ }\mu\text{f}$. Assume $V = 20 \text{ V}$. [6]

Or

8. (a) Explain successive approximation type ADC with neat block diagram. An 8-bit ADC output all 1's, when $V_i = 5.1$ V. Find its : [8]
- (i) Resolution
- (ii) Digital output, when $V_i = 1.28$ V.
- (b) Explain various power supply performance parameters. [5]