

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[4857]-1046

**S.E. (Electronics/E&TC Engineering)**  
**(Second Semester) EXAMINATION, 2015**  
**INTEGRATED CIRCUITS**  
**(2012 PATTERN)**

**Time : Two Hours**

**Maximum Marks : 50**

- N.B. :-** (i) Neat diagrams and waveforms must be drawn wherever necessary.  
(ii) Figures to the right side indicate full marks.  
(iii) Use of calculator is allowed.  
(iv) Assume suitable data if necessary.

1. (a) The following specifications are given for the DIBO differential amplifier : [6]  
 $R_E = 4.7 \text{ k}\Omega$ ,  $R_C = 2.2 \text{ k}\Omega$ ,  $R_{in1} = R_{in2} = 50 \Omega$ ,  
 $V_s = \pm 10 \text{ V}$  and the transistor with  $\beta_{ac} = \beta_{dc} = 100$  with  
 $V_{BE} = 0.7 \text{ V}$ .  
(i) Determine the  $I_{CQ}$  and  $V_{CEQ}$  values.  
(ii) Determine the voltage gain.  
(b) With neat circuit, explain the dominant pole frequency compensation technique. [6]

*Or*

2. (a) Design a DIBO differential amplifier with a constant current bias using diodes to satisfy the following requirements :[6]  
Differential voltage gain  $A_d = \pm 10$   
Current supplied by the constant current bias circuit = 4 mA  
Supply voltage  $V_s = \pm 12 \text{ V}$   
(b) Write a note on noise in op-amp. [6]

P.T.O.

3. (a) Explain virtual ground concept and virtual short concept. [6]  
(b) With neat circuit diagram and waveforms, explain working of half wave precision rectifier. [6]

*Or*

4. (a) Explain sample and hold circuit using op-amp. [6]  
(b) What are the limitations of ideal integrator ? How are they overcome in practical integrators ? [6]

5. (a) With neat circuit diagram, explain current to voltage converter. [5]  
(b) Draw the neat circuit diagram of R-2R ladder digital to analog converter (DAC) and explain its working. [5]  
(c) What output voltage would be produced by a D/A converter whose output range is 0 to 10 V and input binary number is : [3]

(i) 10 (for a 2-bit DAC converter)

(ii) 0110 (for a 4-bit DAC)

(iii) 10111100 (for a 8-bit DAC).

*Or*

6. (a) Explain the operation of successive approximation type analog to digital converter. [5]  
(b) With neat circuit diagram, explain V to I converter with grounded load. [5]  
(c) List various specifications of ADC. [3]

7. (a) Explain the following : [10]  
(i) Digital phase comparator used in PLL  
(ii) PLL as a FSK demodulator.

- (b) For LM317 adjustable voltage regulator,  $R_1 = 240 \Omega$  and  $R_2 = 2 \text{ k}\Omega$ . If  $I_{\text{adj}} = 50 \mu\text{A}$  and  $V_{\text{ref}} = 1.25 \text{ V}$ . Find value of  $V_o$ . [3]

*Or*

8. (a) Define the following terms with reference to PLL : [10]
- (i) Free running frequency
  - (ii) Lock range
  - (iii) Capture range
  - (iv) Pull-in-time.
- (b) Explain low drop-out regulator. [3]