

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[5252]-136

**S.E. (Electronics/Electronics & Telecommunication)**

**(Second Semester) EXAMINATION, 2017**

**INTEGRATED CIRCUITS**

**(2012 PATTERN)**

**Time : Two Hours**

**Maximum Marks : 50**

**N.B. :—** (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6  
and Q. 7 or Q. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Use of electronic pocket calculator is allowed.

(v) Assume suitable data, if necessary.

1. (a) Derive the expression for  $A_v$ ,  $R_i$  and  $R_o$  for dual input balanced output difference amplifier using  $r$ -parameters. [6]

(b) Define and explain the following terms with respect to Op-Amp: PSRR, CMRR, Gain bandwidth product. [6]

*Or*

2. (a) What is the need of frequency compensation? Explain pole zero method of external frequency compensation. [6]

(b) With neat diagram explain the necessity and working of current mirror circuit. [6]

P.T.O.

3. (a) What are problems associated with the ideal integrator ? Draw neat circuit diagram of practical integrator. Explain its operation with its frequency response. [6]
- (b) Draw and explain difference amplifier using Op-amp. Derive the expression for its output voltage. [6]

*Or*

4. (a) Explain the necessity of Precision rectifier and explain the operation of Full wave Precision rectifier with neat circuit diagram. [6]
- (b) Draw and explain Sample and Hold circuit using Op-amp. Explain the necessity of Sample and Hold circuit. [6]
5. (a) With the help of neat diagram explain the operation of R-2R ladder type of DAC. [7]
- (b) Draw neat diagram and V to I convertor with grounded load and explain its operation. [6]

*Or*

6. (a) Calculate output voltage of 6-bit DAC for digital input 100000, 111111 and 111100 with reference voltage of 5V. [6]
- (b) With the help of neat diagram explain the operation of Dual Slope ADC. [7]

7. (a) Explain operation of PLL with the help of neat block diagram. Define the terms Lock range and Capture range. [7]
- (b) Draw neat diagram and explain three-terminal adjustable voltage regulator with expression for output voltage. [6]

*Or*

8. (a) Draw and explain circuit of FM demodulator using PLL. [7]
- (b) Explain low drop out voltage regulator. [6]