

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5352]-163

S.E. (Computer Engineering) (I Sem.) EXAMINATION, 2018
DIGITAL ELECTRONICS AND LOGIC DESIGN
(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B. :—** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.
(ii) Figures to the right indicate full marks.
(iii) Assume suitable data, if necessary.

- Q1) a) Minimize the following function using K-map & realize using Logic gates. [4]
 $F(A,B,C,D) = \sum m(1,5,7,13,15) d(0,6,12,14)$
b) Convert following : [2]
 $(46)_{10} = (?)_8$
c) List the differences between CMOS and TTL [6]

OR

- Q2) a) Convert the following numbers into binary numbers. [4]
i) $(37)_8$ ii) $(25.5)_{10}$
b) Explain standard TTL Characteristics in detail [6]
c) Represent the following signed number in 2s complement method: [2]
i) +25 ii) -25
Q3) a) Design a 3-bit Excess 3 to 3-bit BCD code converter using logic gate. [6]
b) Design Mod-5 synchronous counter using JK FFs. [4]
c) Draw the excitation table of J-K Flip-flop. [2]

P.T.O.

OR

- Q4) a) Design a 4-bit Binary to Gray code converter circuit using logic gates [4]
b) Design a Mod 20 counter using decade counter IC 7490 [6]
c) Perform the following: [2]
 $(11011)_2 + (0101)_2 = (?)_2$
- Q5) a) State and explain basic component of ASM chart? Also explain the Salient features of ASM chart? [7]
b) Write VHDL code 4:1 Multiplexer using Behavioral and Dataflow modeling style. [6]

OR

- Q6) a) Design a sequence generator circuit to generate the sequence 1-2-3-7-1 using Multiplexer Controller based ASM approach. [7]
Consideration :
i) If control input C = 0, the sequence generator circuit in the same state.
ii) If control input C = 1, the sequence generator circuit goes into next state.
- b) Explain the following statements used in VHDL with suitable examples: [6]
i) CASE.
ii) With - Select - When.
iii) Loop statement.
- Q7) a) Comparison between PROM, PLA and PAL [7]
b) Draw and explain the basic architecture of FPGA. [6]

OR

- Q8) a) A combinational circuits is defined by the function [7]
 $F_1(A,B,C) = \sum m(0,1,3,7)$
 $F_2(A,B,C) = \sum m(1,2,5,6)$
Implement this circuit with PLA.
- b) A combinational circuits is defined by the function [6]
 $F_1(A,B,C) = \sum m(0,1,5,6,7)$
Implement this circuit with PAL.