

Total No. of Questions : 10]

SEAT No. :

**P2389**

**[4758] - 548**

[Total No. of Pages :2

**T.E. (Electrical)**

**POWER ELECTRONICS**

**(2012 Course) (End - Sem.) (Semester - I)**

*Time : 2½ Hours]*

*[Max. Marks : 70*

*Instructions to the candidates:*

- 1) *Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8, Q9 or Q10.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Assume Suitable data if necessary.*

**Q1) a)** What type of triggering is used in SCRs? Explain R & RC triggering. **[5]**

b) Explain characteristics of GTO. **[5]**

OR

**Q2) a)** Explain over voltage & over current protections for SCR. **[5]**

b) For 1ph full controlled bridge rectifier, calculate rectification efficiency, for Resistive load. **[5]**

**Q3) a)** Explain working of Triac as light dimmer switch. **[5]**

b) What is current source converter? Explain its operation. **[5]**

OR

**Q4)** Explain operation of 3ph half controlled bridge converter feeding RL load. Draw output voltage waveform for  $\alpha = 30^\circ$  & write output voltage expression. **[10]**

**Q5) a)** Draw VI chara. of MOSFET & explain its control. **[8]**

b) Draw step down chopper circuit & explain with expression for output voltage interms of control parameter. **[8]**

OR

*P.T.O.*

- Q6)** a) Explain VI chara. of MCT & give applications. [8]
- b) A step down chopper feeding load with  $R = 10\Omega$  and  $L = 5 \text{ mH}$  from 220V supply at 500 Hz and 30% duty. Calculate average output voltage and av. current. Find  $I_{\max}$  &  $I_{\min}$  if % ripple is 10%. [8]

- Q7)** a) Explain 1ph. full bridge voltage source inverter. Derive output voltage expression for RL load. Draw relevant waveforms. [8]
- b) Explain Sinusoidal PWM Technique for Inverters. Using 5 pulses /half cycle. Comment on harmonics in output voltage. [8]

OR

- Q8)** a) Explain working of 1ph full bridge inverter generating quasisquare wave in output, across inductive load. Draw waveform & explain. [10]
- b) Explain Multiple pulse PWM used in inverters. What is its advantage over single pulse PWM? [6]

- Q9)** a) Explain 3ph.  $120^\circ$  mode conduction VSI operation with control signals & output phase voltage waveforms for 3ph. resistive star connected load. [10]
- b) Explain voltage control & harmonic elimination techniques used in inverters. [8]

OR

- Q10)** a) Explain cascaded Multilevel inverter using 3H- bridges connected to V input supply. Draw output voltage waveforms. [10]
- b) Compare: [8]
- Multipulse and Multi level inverters.
  - VSI & CSI.

