

Total No. of Questions : 10]

SEAT No. :

**P2587**

**[5153]-563**

[Total No. of Pages : 2

**T.E. (Electrical)**

**POWER ELECTRONICS**

**(2012 Pattern) (Semester-I)(EndSem.)**

*Time : 2½ Hours]*

*[Max. Marks :70*

*Instructions to candidates:*

- 1) *Solve Questions 1 or 2, Question 3 or 4, Question 5 or 6, Question 7 or 8, Question 9 or 10.*
- 2) *Assume Suitable data, if necessary.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Figures to the right indicate full marks.*

**Q1) a)** Draw neat circuit diagram and explain working of single phase fully controlled bridge converter feeding RL load with Free Wheeling Diode. Draw waveforms of load voltage, load current. **[6]**

b) Explain the difference between SCR and GTO. **[4]**

OR

**Q2) a)** Draw neat circuit diagram for a 1 phase semi controlled converter feeding R-L load at  $\alpha=60^\circ$ . Draw output voltage waveform showing devices conducting during one cycle of input ac voltage. **[6]**

b) Draw a neat circuit diagram of a simple light dimmer circuit using Triac and draw the waveforms of voltage across the bulb and current passing through it for  $\alpha=90^\circ$ . **[4]**

**Q3)** For a 3 phase fully controlled Bridge converter feeding resistive load. **[10]**

- a) Draw neat circuit diagram and explain working
- b) Draw output voltage and current waveforms at  $\alpha=60^\circ$
- c) Write the switching sequence of SCRS clearly
- d) Derive expression for average output voltage.

OR

**Q4) a)** Describe the RC full wave trigger circuit for one SCR when the load is AC. Draw related voltage waveforms. **[4]**

b) Explain with circuit diagram and waveforms working of 2 stage sequence control of AC regulator. **[6]**

**P.T.O.**

- Q5)** a) What is time ratio control in D.C. choppers? Explain the use of TRC for controlling the output voltage in choppers. [8]  
b) Give comparison between MOSFET and IGBT [8]

OR

- Q6)** a) Explain with a diagram step-up chopper and derive the expression for the output voltage. A step up chopper with a pulse width of  $150 \mu s$  is operating on 220 V dc supply. Compute the load voltage if the blocking period of the device is  $40 \mu s$ . [8]  
b) Explain output and Transfer characteristics of IGBT [8]

- Q7)** a) With a neat circuit diagram and necessary waveforms explain working of single phase full bridge voltage source inverter with inductive load. [8]  
b) Why voltage control is needed in inverter circuits? State the various methods of voltage control in inverters circuits and explain any two methods. [8]

OR

- Q8)** a) With a neat circuit diagram explain the working of single phase capacitor commutated current source inverter with resistive load. Draw also the related voltage and current waveforms. [8]  
b) Explain single pulse width modulation with diagrams. Derive an expression for output voltage. [8]

- Q9)** a) Explain working of three phase inverter in  $120^\circ$  mode of operation. For star connected load draw output voltage waveforms. Show devices conducting in each step. [12]  
b) Compare Current Source Inverter and Voltage Source Inverter. [6]

OR

- Q10)** a) State the need of multilevel inverters. Explain the cascaded multilevel inverters with the help of neat circuit diagram and necessary waveform. [12]  
b) Compare multilevel inverter with multi pulse inverter. [6]

