

Total No. of Questions : 6]

SEAT No. :

P5030

[Total No. of Pages : 2

**TE / Insem - 528**  
**T.E. (Electrical)**  
**POWER ELECTRONICS**  
**(2012 Pattern)**

*Time : 1 Hour]*

*[Max. Marks :30*

*Instructions to the candidates:*

- 1) *Solve Q.1 or Q.2 Q.3 or Q.4 Q.5 or Q.6.*
- 2) *Neat diagram must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of calculator is allowed.*
- 5) *Assume suitable data if necessary.*

- Q1)** a) Define latching and holding currents in the context of SCR. Show these currents on its static I -V characteristics. **[5]**
- b) State the turn on methods of thyristor. Explain the method which is commonly used. **[5]**

OR

- Q2)** a) Explain the difference between an SCR and GTO. **[5]**
- b) Explain the over current and thermal protection of SCR. **[5]**
- Q3)** a) Explain I phase fully controlled bridge converter with R load and draw output voltage waveforms for firing angle of 60 degrees. **[6]**
- b) Derive the expression of output voltage of single phase fully controlled converter by taking into account the effect of source inductance. **[4]**

OR

- Q4)** a) Draw neat circuit diagram for a 1phase semi controlled converter feeding R-L load at  $\alpha = 30^\circ$ . Draw output voltage waveform showing devices conducting during one cycle of input ac voltage. **[6]**
- b) Draw neat circuit diagram and explain working of single phase fully controlled bridge converter feeding RL load with free wheeling diode **[4]**

**P.T.O**

**Q5)** For a 3 phase fully controlled bridge converter feeding resistive load

- a) Draw neat circuit diagram [1]
- b) Draw output voltage and current waveforms at  $\alpha = 30^\circ$  [4]
- c) Write the switching sequence of SCRS clearly [3]
- d) Derive expression for average output voltage [2]

OR

**Q6)** a) Explain application TRIAC as a light dimmer switch [5]

b) For a single phase full wave A.C. voltage regulator with R load

- i) Draw circuit diagram [1]
- ii) Draw output voltage waveform at firing angle  $45^\circ$  [2]
- iii) Derive the formula for rms output voltage [2]

