

Total No. of Questions : 6]

SEAT No. :

P5640

TE/INSEM./OCT.-28

[Total No. of Pages : 2

T.E. (Electrical)

POWER ELECTRONICS

(2012 Course) (303143) (Semester - I)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q1 or Q2, Q3 or Q4, Q5 or Q6.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.
- 4) Assume suitable data, if necessary.

UNIT - I

- Q1)** a) Compare the characteristics of an Ideal switch with Practical switch characteristics. [5]
b) Explain latching of SCR using two transistor analogy. How duration of gate pulse is decided? [5]

OR

- Q2)** a) Draw Dynamic characteristics of SCR and Explain turn on and turn off times. [5]
b) List various Protections used for SCR and Explain. [5]

UNIT - II

- Q3)** a) With help of a neat diagram and waveforms for output voltage and voltage across switch, explain the working of a single phase fully controlled bridge converter feeding RL load assuming continuous conduction. [6]
b) A single phase semi converter delivers power to RLE load with $R = 5$ ohm, $L = 10\text{mH}$ and $E = 80\text{V}$. The ac supply voltage is $230\text{V}, 50\text{Hz}$. For the continuous conduction, find the average value of output current for a firing angle of 50 deg. [4]

OR

- Q4)** a) With help of a neat diagram and waveforms explain the working of a single phase dual converter. [5]
b) A single phase full converter is supplied from $230\text{ V}, 50\text{ Hz}$ source having the source inductance of 0.1 mH . If average load current is 150 A . For a firing angle delay of 30 deg, find the average output voltage and the angle of overlap. [5]

P.T.O.

UNIT - III

- Q5)** a) For a three phase fully controlled bridge converter, derive average voltage expression for resistive load. What is the condition for continuous current. Draw the waveform. [6]
- b) Explain four quadrant operation of TRIAC using neat diagram. [4]

OR

- Q6)** a) Explain working of single phase ac regulator feeding RL load. Draw output voltage waveform. [5]
- b) A fully controlled 3 phase bridge converter is supplied from 200 V line voltage to feed highly inductive load with $R = 10 \text{ ohm}$ at firing angle of 45 degree. Calculate the average load voltage and average load current. [5]

