

Seat  
No.

**T.E. (Electrical)(Semester – I) Examination, 2014**  
**POWER ELECTRONICS**  
**(2012 Course)**

Time : 3 Hours

Max. Marks : 70

1. a) For SCR, account for switching losses and effect of switching frequency on power loss. 5

- b) Explain 'dynamic chara' of SCR. 5

OR

2. a) Explain single phase dual converter with circulating current mode. 5

- b) Explain single phase ac regulator feeding RL load. Draw output voltage waveform. 5

3. a) Compare output voltages available from 1ph and 3 ph. fully controlled bridge rectifiers based on magnitude, ripple content and ripple frequency. 5

- b) Explain use of diode as FWD and feedback diode for inductive loads. 5

OR

4. a) Draw and explain gate chara of SCR. 5

- b) Explain 3 ph. semicontrolled rectifier feeding RL load. Write output voltage expression. 5

5. a) Explain Type C chopper operation with circuit diagram and waveforms. 8

- b) Compare MOSFET, IGBT and power transistor with neat symbols and SOAs 8

OR

6. a) Draw VI chara of MCT and explain operation. 8

- b) For a chopper feeding inductive load with  $R = 4\Omega$  &  $L = 6 \text{ mH}$  from 200 V source at 50% duty and  $1\text{kH}_2$  switching frequency, find

- Maxi and Mini load current
- Peak to Peak ripple current
- Av. voltage and Av. load current.

7. a) Explain working of 1ph bridge inverter feeding RL load. Draw voltage and current waveforms and comment on need for feedback diodes. 8

- b) Explain multiple pulse width Modulation Technique for Inverter control. Explain modulation indices and effect on harmonic control. 8

OR

8. a) Explain why quasi square output voltage has better performance than square wave output.  
How 1ph. inverter bridge can be operated to give quasi square output ? 8

- b) Explain sinusoidal PWM technique for inverters. How voltage and freq. control is achieved ? 8

P.T.O.



9. a) Draw 3 ph inverter bridge to feed 3 ph resistive load (star connected) using  $180^\circ$  mode of conduction. Draw control signals for devices used and output phase and line voltage. **10**
- b) Compare CSI and USI based on working and advantages. **8**
- OR
10. a) What is the need of using multilevel inverters ? Explain one type of multilevel inverter. **10**
- b) Compare and comment on Multipulse and Multilevel inverter output voltages. **8**