

Total No. of Questions : 10]

SEAT No. :

P1710

[5058]-343

[Total No. of Pages : 2

T.E. (Electrical)

POWER ELECTRONICS

(2012 Course) (Semester - I)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8, Q.9 or Q.10.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.

- Q1)** a) Describe working of single phase bridge converter with R load Draw waveforms of load voltage, load current. [5]
b) How ac voltage regulators are classified? Explain single phase ac regulator feeding inductive load. Draw output voltage waveform. [5]

OR

- Q2)** a) Draw & Explain Gate Characteristic of SCR. [5]
b) Explain the following ratings of the thyristor. [5]
i) Latching current
ii) Holding current

- Q3)** a) Explain working of three phase full converter with a firing angle of 30° & obtain expression for phase voltage & Line voltage. [5]
b) State and explain the effect of source inductance on operation of converter. [5]

OR

- Q4)** a) Draw and explain single phase semi converter with output waveforms with RL load. [5]
b) Explain R-C triggering circuit of Thyristor. [5]

- Q5)** a) Explain Class E chopper feeding RLE load in detail. [8]
b) Describe the basic structure of MCT. Give its equivalent circuit and explain the turn on and turn off process. [8]

OR

P.T.O.

- Q6)** a) What is time ratio control in dc choppers? Explain the use of TRC for controlling the output voltage in choppers. [8]
b) For Type A chopper the supply voltage is 230V, load resistance being 10Ω for the duty cycle of 40%. Find the average and rms values of the output voltage and chopper efficiency by taking voltage drop of 2V across the chopper during ON condition. [8]

- Q7)** a) Explain with circuit diagram and waveforms operation of single phase current source inverter. [8]
b) Explain Sinusoidal Pulse width modulation with necessary waveforms. [8]

OR

- Q8)** a) Explain with circuit diagram and waveforms operation of single phase current source inverter. [8]
b) Derive expression for output voltage in single pulse Modulation by Fourier analysis. [8]

- Q9)** a) Explain working of three phase six step voltage source inverter in 120° mode of operation. For star connected load draw output voltage waveforms. Show devices conducting in each step. [10]
b) Compare Multilevel inverter and Multi Pulse Inverter. [8]

OR

- Q10)** a) Draw neat diagram and explain cascaded multilevel inverter. [8]
b) Explain working of three phase six step voltage source inverter in 180° mode of operation. For star connected load draw output voltage waveforms. Show devices conducting in each step. [10]

